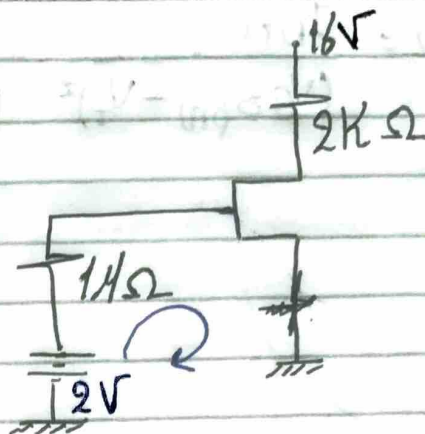


$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2$$

Sec 20-
lec 20

ex: $V_p = -8V$
 $I_{DSS} = 10mA$



* Determine the transfer characteristic curve.

2) I_{DQ}

$$V_S = 0 \quad \therefore V_{GS} = V_G - V_S = V_G$$

$$2 = I_G R_G + V_{GS}$$

$$* V_{GS} = V_p \left(1 - \sqrt{\frac{I_D}{I_{DSS}}}\right)$$

$$2 = V_G + V_G \quad \therefore 2 = 2V_G \quad \therefore V_G = 1V$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2$$

MOSFET:-
Depletion.

Enhancement
* MOSFET

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2$$

$$I_D = K (V_{GS} - V_t)^2$$

$$K = \frac{I_{D(on)}}{(V_{GS(on)} - V_t)^2}$$

* $V_{GS(on)}$


* $V_{GS(th)}$

Data: $V_{GS(on)} = 10V$, $I_D(on) = 3mA$, $V_{GS(th)} = 3V$

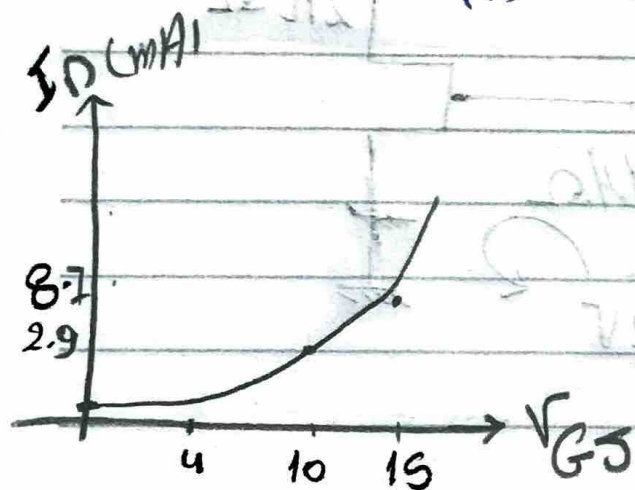1) k , 2) the transfer characteristic

Sol

$$k = \frac{I_{D(on)}}{(V_{GS(on)} - V_t)^2} = \frac{3 \times 10^{-3}}{(10 - 3)^2} = 0.061 A/V^2$$



جرف

$$*I_D = k(V_{GS} - V_t)^2$$

V_{GS}	I_D
4	0.061 mA
10	2.9 mA
15	8.7 mA
20	17.6 mA

Main differences between the FET and BJT :-

- * the BJT transistor is a current-controlled device,
- * The FET Transistor is a voltage-controlled device.


* the BJT → bipolar electrons and holes

* the FET → unipolar electrons or holes

FET



(JFET)

(MOSFET)

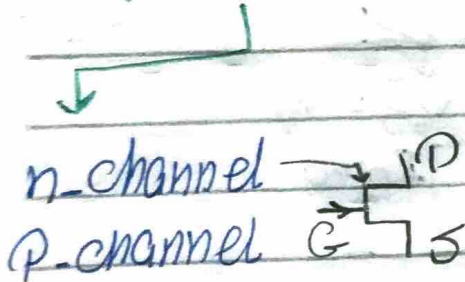


(Enhancement)

(Depletion)

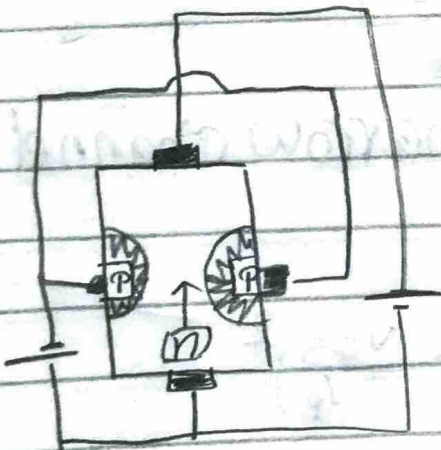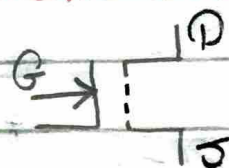


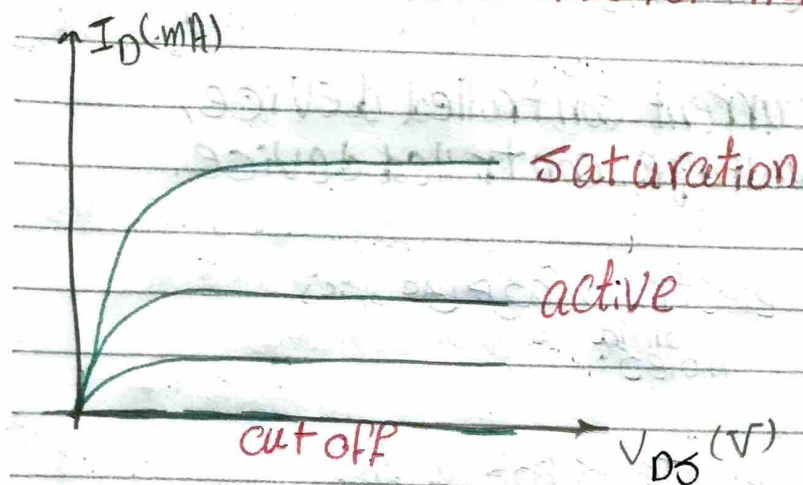* Characteristics curve for n-channel JFET




$$* I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2$$
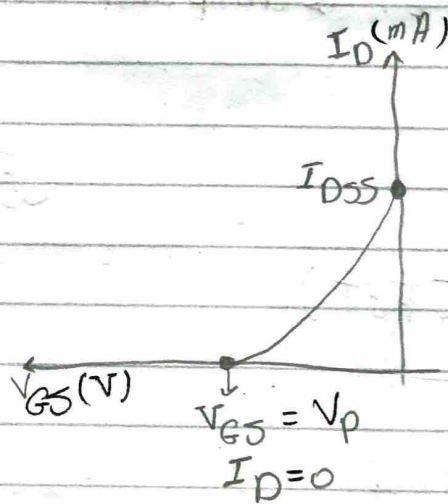
$$V_{GS} = V_p \left(1 - \sqrt{\frac{I_D}{I_{DSS}}}\right)$$



* Depletion Type MOSFET :-

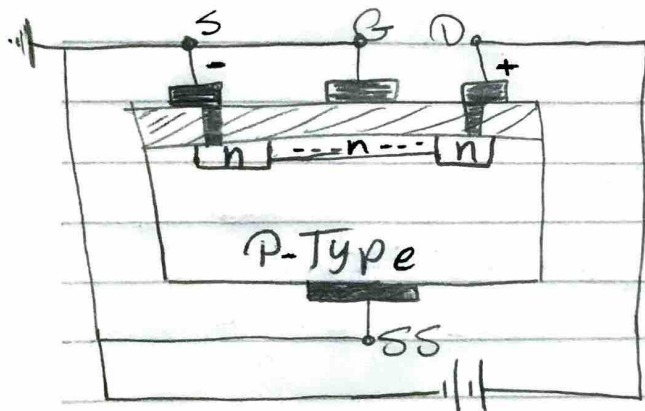
- * The gate current (I_G) is essentially zero
- * The drain and source connected by a narrow channel.



$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2$$

characteristics curve for n-channel D-MOSFET

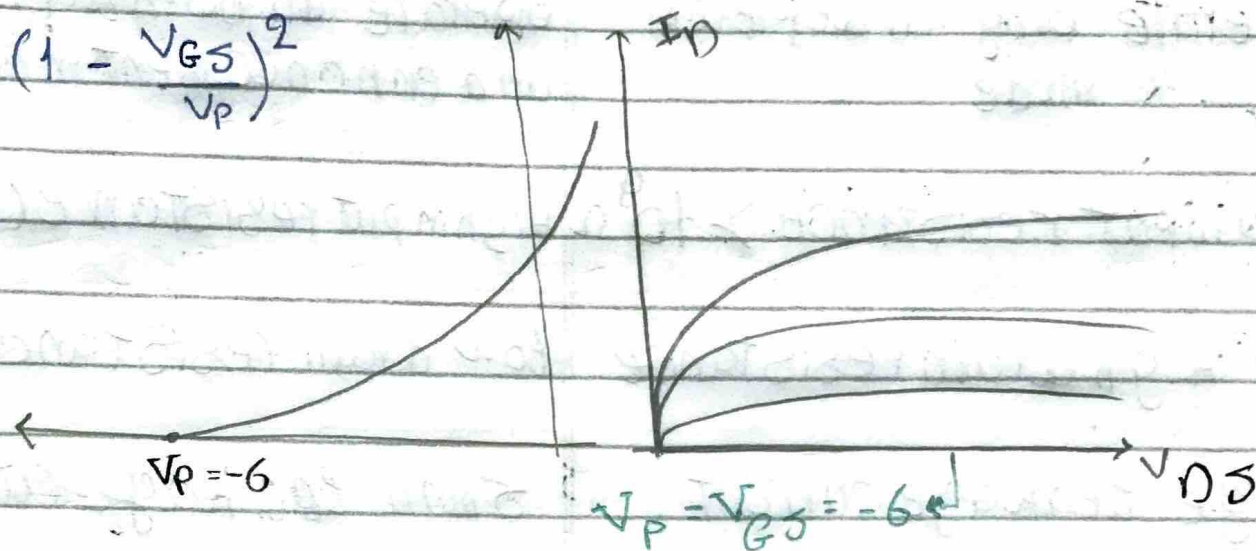
$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$



* Enhancement MOSFET :-

$$I_D = K (V_{GS} - V_t)^2$$
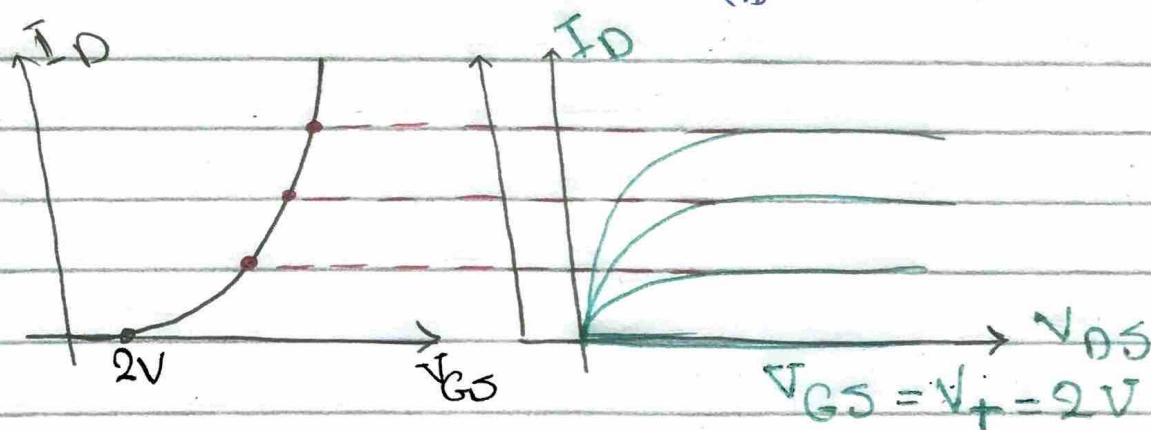
$$* K = \frac{I_{D(on)}}{(V_{GS(en)} - V_t)^2}$$



JFET

operate only in depletion mode

low input resistance $> 10^9 \Omega$

~~to~~ High drain resistance

large leakage current

Not easy construction

MOSFET

operate on both depletion and enhancement mode

High input resistance ($10^{13} \Omega$)

low drain resistance

small leakage current

easy construction