


El-Manzala Higher Institute for Engineering and Technology		
First Semester :2023/2024	Code: : COM 121	
Course title: Electronic Engineering	Dr. Basma Yusef	
Sheet (1)	Eng. Madleen Mohamed	

Question (1):


Using the data provided on the specification sheet of Fig. 5.39 and an average thresh-old voltage of  $V_{GS(Th)} = 3\text{ V}$ , determine:

- The resulting value of  $k$  for the MOSFET.
- The transfer characteristics.

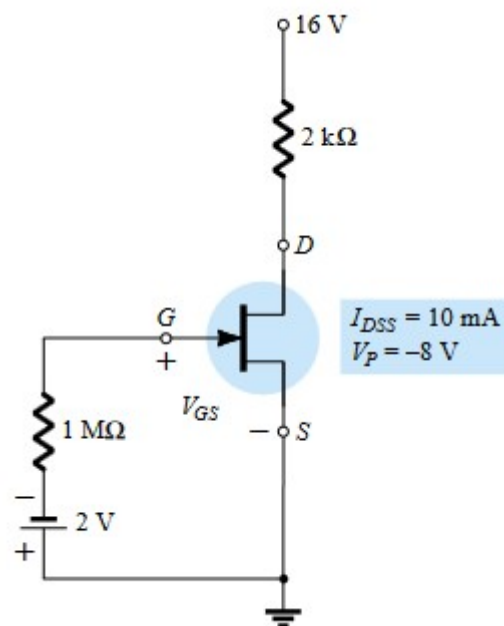Question (2):

Determine the following for the network of figure.


- $V_{GS}$  Q. (b)  $I_D$  Q.(c)  $V_{DS}$ . (d)  $V_D$ . (e)  $V_G$ .



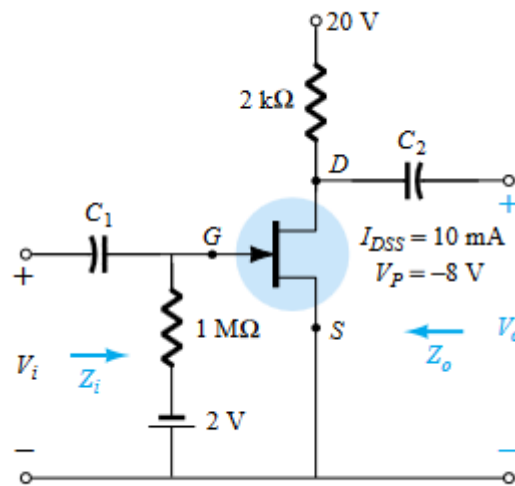Question (3):

The fixed-bias configuration of Example 6.1 had an operating point defined by  $V_{GS_Q} = -2\text{ V}$  and  $I_{D_Q} = 5.625\text{ mA}$ , with  $I_{DSS} = 10\text{ mA}$  and  $V_P = -8\text{ V}$ . The network is redrawn as Fig. 9.14 with an applied signal  $V_i$ . The value of  $y_{os}$  is provided as  $40\text{ }\mu\text{S}$ .

- Determine  $g_m$ .
- Find  $r_d$ .
- Determine  $Z_i$ .
- Calculate  $Z_o$ .
- Determine the voltage gain  $A_v$ .
- Determine  $A_v$  ignoring the effects of  $r_d$ .



Question (4):

The self-bias configuration of Example 6.2 has an operating point defined by  $V_{GS_Q} = -2.6$  V and  $I_{D_Q} = 2.6$  mA, with  $I_{DSS} = 8$  mA and  $V_P = -6$  V. The network is redrawn as Fig. 9.20 with an applied signal  $V_i$ . The value of  $y_{os}$  is given as  $20 \mu\text{S}$ .

- Determine  $g_m$ .
- Find  $r_d$ .
- Find  $Z_i$ .
- Calculate  $Z_o$  with and without the effects of  $r_d$ . Compare the results.
- Calculate  $A_v$  with and without the effects of  $r_d$ . Compare the results.

