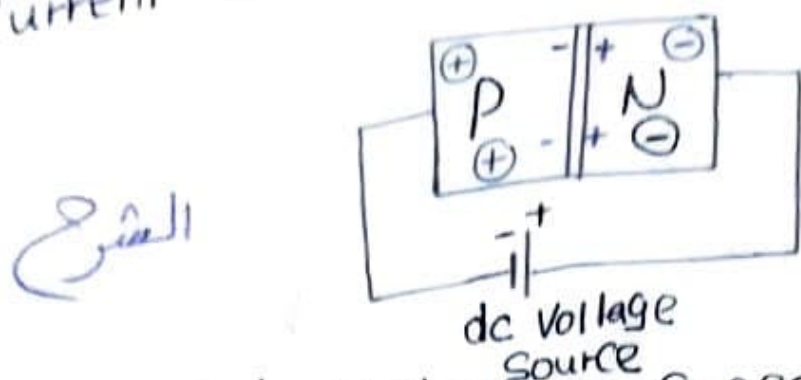


Reverse Bias

- ① Apply dc Voltage across Diode
- ② Current will not flow through P-N junction



- ① When (-) of dc Voltage is connected to P-region and (+) of dc Voltage is connected to N-region, the junction Diode is reverse biased.
- ② (+) of dc Voltage Pulls the Free electrons which are the majority Carriers in N-region away from the P-N junction because unlike charges attract.
- ③ electrons Flow toward the Positive side of dc Voltage additional Positive ions are Created.
- ④ Width of depletion region increase.
- ⑤ Current will Not Flow Through P-N junction.


Forward Bias	Reverse Bias
Diode → short Circuit with 0.7 volt and 0.3 (Ge)	Diode → open Circuit

- 1] Discuss the Working of a P-N junction diode under Forward and reverse biasing. Draw I-V Characteristic Curve of the junction Diode.

Forward Bias

① Apply dc voltage across Diode.

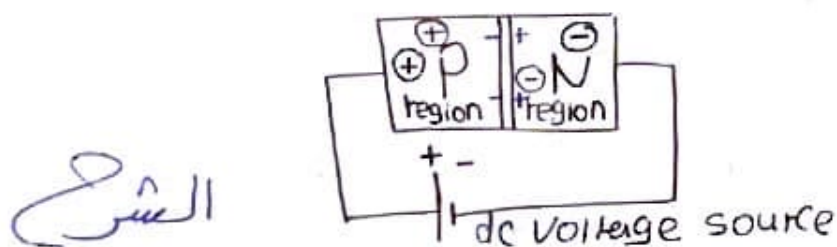② Current will flow through the P-N junction.



- ① When (-) of dc voltage is connected to N region and (+) of dc voltage is connected to P region, the junction Diode is Forward biased.
- ② (-) of dc voltage Pushes the Free electrons which are the majority Carriers in N-region toward P-N junction because the Like charges repel.
- ③ The voltage source provides Sufficient energy to Free electrons to overcome the barrier of depletion region and move on through the P region
- ④ Current will flow through P-N junction and the Circuit.



$$V_{\text{ripple P-P}} = \frac{1}{\text{FRC}} (V_{\text{Peak}})$$

$$V_{\text{ripple}} =$$


$$\frac{V_{\text{Peak}}}{2\text{FRC}}$$

Ideal Diode

$$V_{\text{ripple}} = \frac{V_{\text{Peak}}}{2\pi\text{RC}}$$

Ideal Diode

I-V
Characteristic Curve of Diode

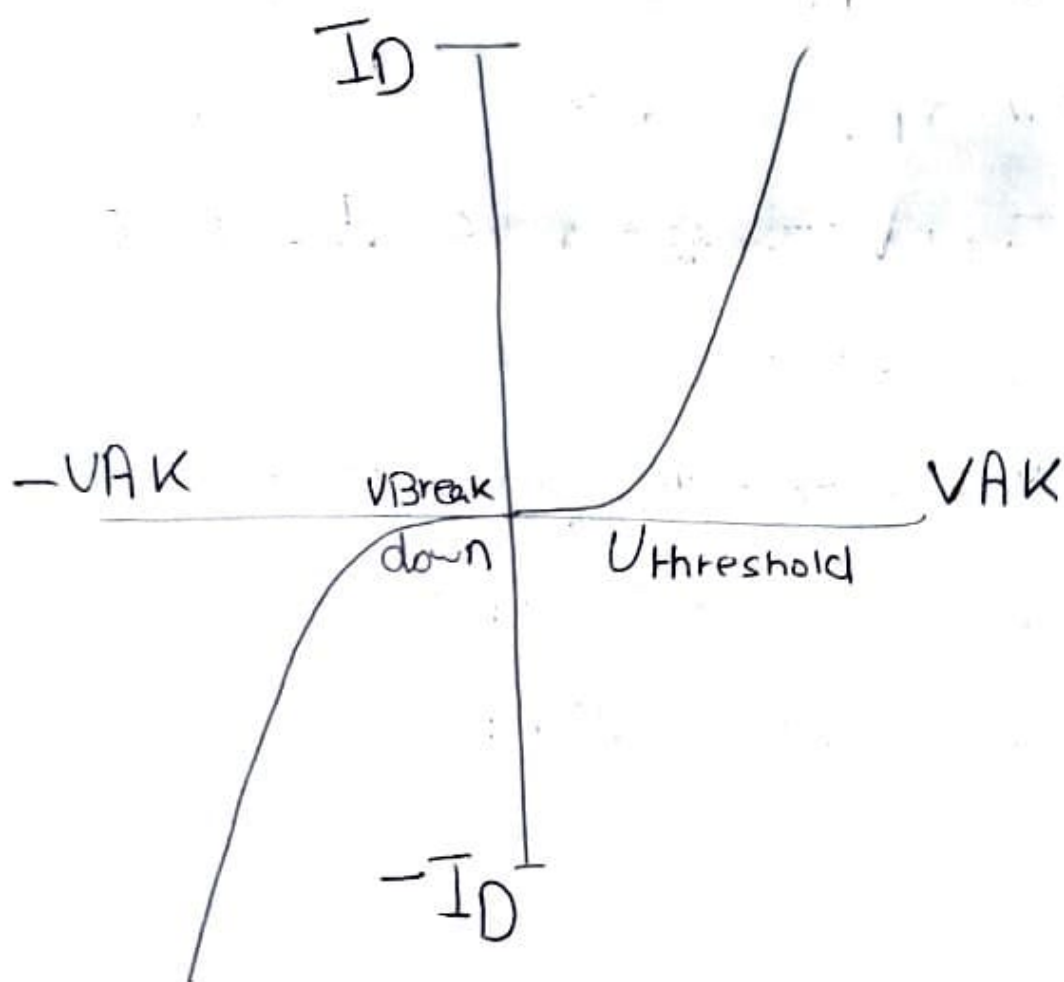

$$V_{out \text{ r.m.s}} = \frac{V_{out \text{ Peak}}}{\sqrt{2}}$$


$$V_{out \text{ Avg}} = \frac{V_{out \text{ Peak}}}{\pi} = V_{out \text{ DC}}$$

$$PIV = V_{out \text{ Peak}}$$


Peak Inverse Voltage

$$\text{out Put Frequency} = 50 \text{ Hz}$$

With Capacitor

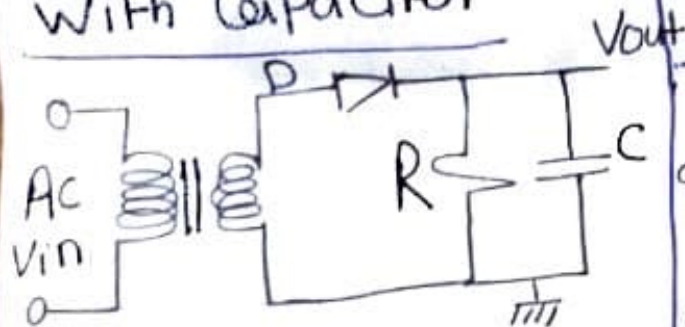


Input Signal

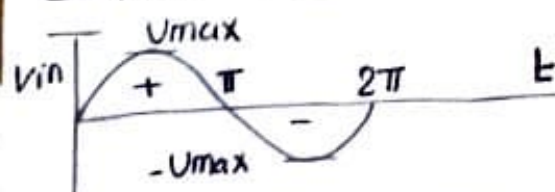

$$\text{Input Frequency} = 50 \text{ Hz}$$

Output Signal

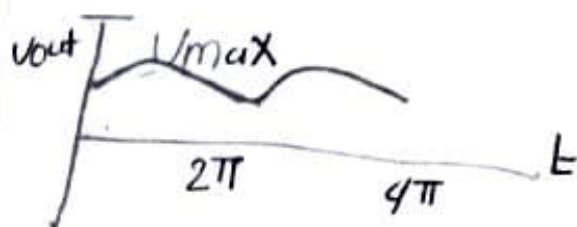

$$V_{\text{ripple}} = V_{\text{Peak}} - V_{\text{dc}}$$

$$V_{out \text{ r.m.s}} = \frac{V_{out \text{ Peak}}}{\sqrt{2}}$$

$$V_{out \text{ Avg}} = \frac{V_{out \text{ Peak}} \times 2}{\pi} = V_{out \text{ DC}}$$

~~PIV~~


at Each Diode

$$PIV(\text{Full wave}) = 2V_{\text{Peak}} + 0.7$$


$$PIV = V_{\text{Peak}} + 0.7$$

at Each Diode

With Capacitor

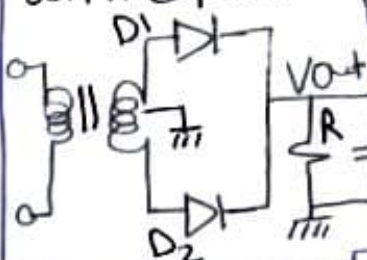


Input Signal

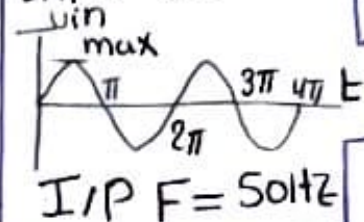

$$I/P F = 50 \text{ Hz}$$


Output Signal

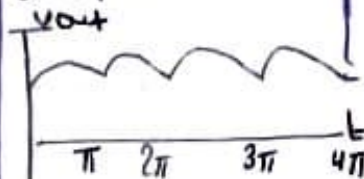


$$O/P F = 100 \text{ Hz}$$

$$V_{\text{ripple}} = V_{\text{Peak}} - V_{\text{dc}}$$

With Capacitor

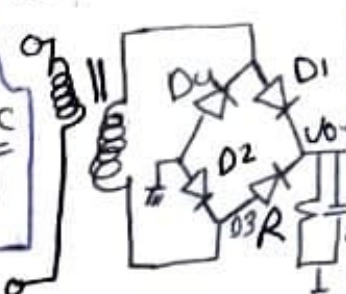

Input Signal

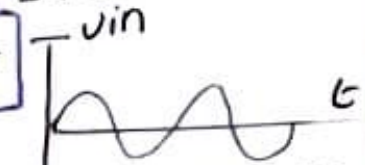

$$I/P F = 50 \text{ Hz}$$

Output Signal




$$O/P F = 100 \text{ Hz}$$


$$V_{\text{ripple}} = V_{\text{Peak}} - V_{\text{dc}}$$

Comparison between Half wave Rectifier and Full wave Rectifier without Capacitor and with Capacitor.

Half wave Rectifier

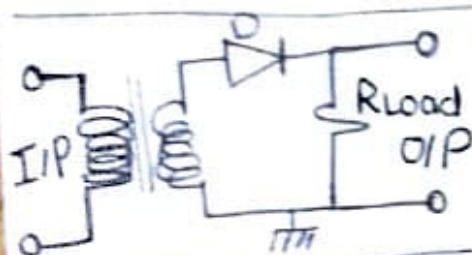


Input Signal

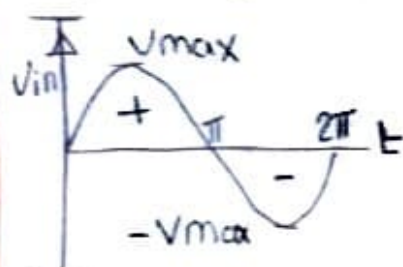

Input Frequency = 50 Hz

Output Signal

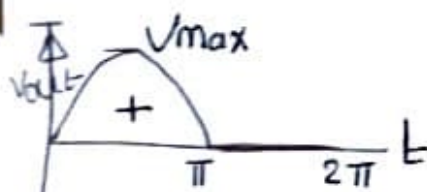

Ideal Case

$$V_{out} = V_{max} = V_{sec}$$


Practical Case

$$V_{out} = V_{sec} - 0.7$$


Peak

Full wave Rectifier

Center tapped

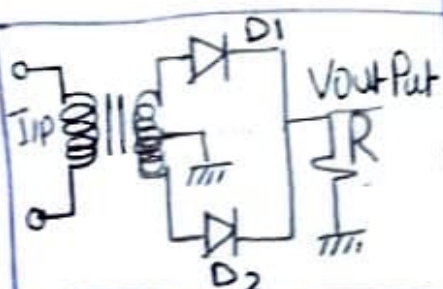


Input Signal

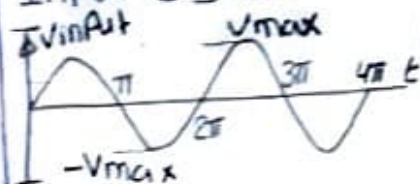

Input Frequency = 50 Hz

Output Signal

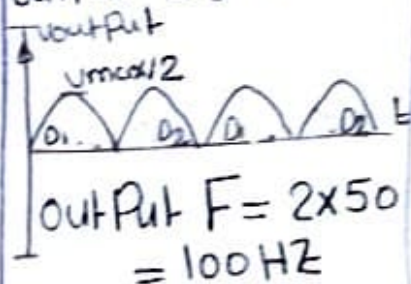

Output $F = 2 \times 50$
= 100 Hz

Ideal Case

$$V_{out} = \frac{V_{sec}}{2}$$


Peak

Practical Case


$$V_{out} = \frac{V_{sec}}{2} - 0.7$$

Peak

Bridge

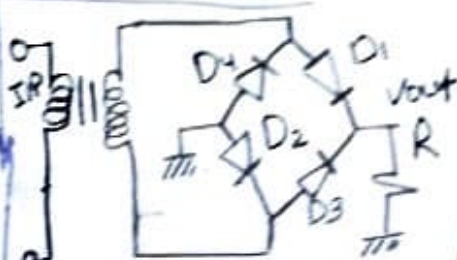


Input Signal

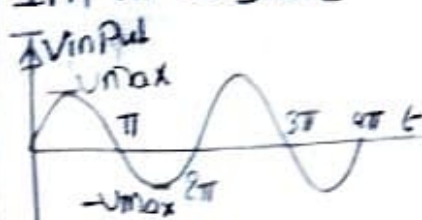

Input Frequency = 50 Hz

Output Signal

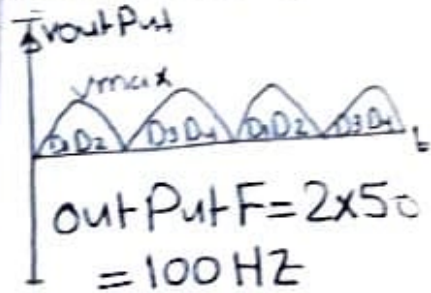

Output $F = 2 \times 50$
= 100 Hz

Ideal Case

$$V_{out} = V_{max}$$

Peak

Practical Case

$$V_{out} = V_{max} - 0.7 \times 2$$

Peak = $V_{max} - 1.4$