


El-Manzala Higher Institute for Engineering and Technology		
First Semester :2023/2024	Code: COM 121	
Course title: Electronic Engineering	Dr. Basma Yusef	
Sheet (2)	Eng. Madleen Mohamed	

Question (1):


Using the data provided on the specification sheet of Fig. 5.39 and an average thresh-ohd voltage of $V_{GS(Th)} = 3\text{ V}$, $V_{GS(on)} = 10$, $I_{D(on)} = 3$ determine:

- The resulting value of k for the MOSFET.
- The transfer characteristics.

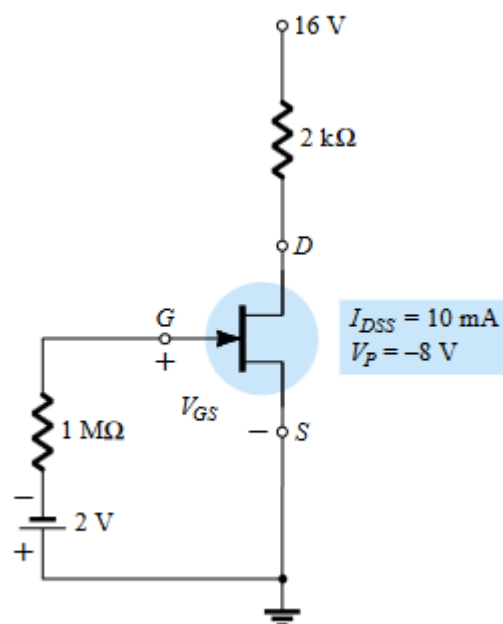Question (2):

Determine the following for the network of figure.


- V_{GS} Q. (b) I_D Q. (c) V_{DS} . (d) V_D . (e) V_G .



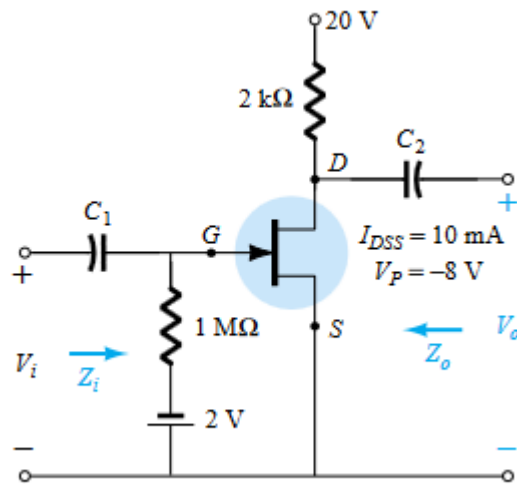Question (3):

The fixed-bias configuration of Example 6.1 had an operating point defined by $V_{GS_Q} = -2\text{ V}$ and $I_{D_Q} = 5.625\text{ mA}$, with $I_{DSS} = 10\text{ mA}$ and $V_P = -8\text{ V}$. The network is redrawn as Fig. 9.14 with an applied signal V_i . The value of y_{os} is provided as $40\text{ }\mu\text{S}$.


- Determine g_m .
- Find r_d .
- Determine Z_i .
- Calculate Z_o .
- Determine the voltage gain A_v .
- Determine A_v ignoring the effects of r_d .



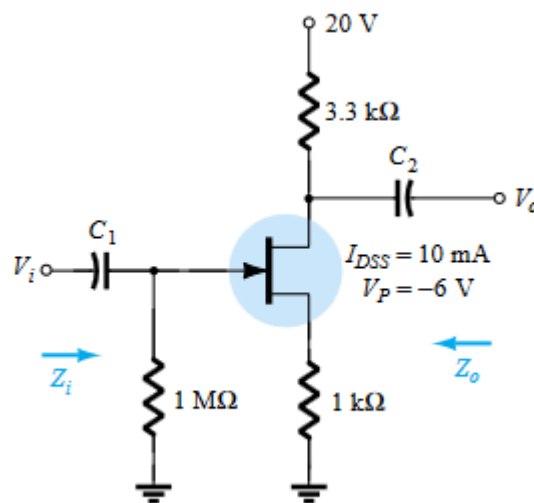Question (4):

The self-bias configuration of Example 6.2 has an operating point defined by $V_{GS_Q} = -2.6$ V and $I_{D_Q} = 2.6$ mA, with $I_{DSS} = 8$ mA and $V_P = -6$ V. The network is redrawn as Fig. 9.20 with an applied signal V_i . The value of y_{os} is given as $20 \mu\text{S}$.

- Determine g_m .
- Find r_d .
- Find Z_i .
- Calculate Z_o with and without the effects of r_d . Compare the results.
- Calculate A_v with and without the effects of r_d . Compare the results.



Question (5):

Sketch the transfer characteristics for an n-channel depletion-type MOSFET with $I_{DSS} = 10$ mA and $V_P = -4$ V.

Question (6):

$I_{D(on)} = 3 \text{ mA}$, $V_{GS(on)} = 10 \text{ V}$, $V_{GS(Th)} = 3 \text{ V}$, determine:

- (a) The resulting value of k for the MOSFET.
- (b) The transfer characteristics

Question (7):

Given $I_D = 14 \text{ mA}$ and $V_{GS} = 1 \text{ V}$, determine V_P if $I_{DSS} = 9.5 \text{ mA}$ for a depletion-type MOSFET.

Question (8):

Given $I_D = 4 \text{ mA}$ at $V_{GS} = -2 \text{ V}$, determine I_{DSS} if $V_P = -5 \text{ V}$.

Question (9):

a) What is the significant difference between the construction of an enhancement-type MOSFET and a depletion-type MOSFET?

b) Given $k = 0.4 \times 10^{-3} \text{ A/V}^2$ and $I_D(on) = 3 \text{ mA}$ with $V_{GS(on)} = 4 \text{ V}$, determine V_T .

c) E-MOSFET of figure $K = 0.24 \times 10^{-3} \text{ A/V}^2$, $V_{GQ} = 6.4 \text{ V}$, and $I_{DQ} = 2.75 \text{ mA}$.

1) Determine g_m

(c) Calculate Z_i with and without r_d . Compare results.

(d) Find Z_o with and without r_d . Compare results.

(e) Find A_v with and without r_d . Compare results.

