




Electronic Engineering COM121



Assist. Prof.
Basma M. Yousef

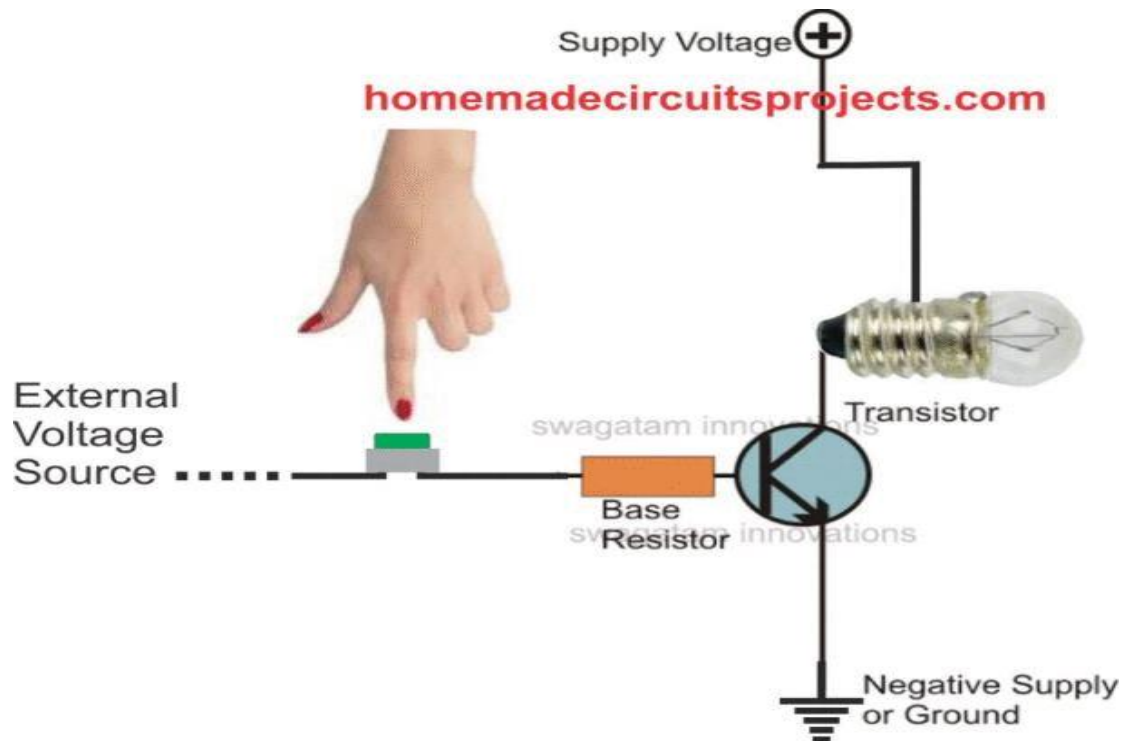- **Amplifiers:** transistors biased in the flat-part of the I-V curves
 - **BJT:** forward-active region
 - **MOSFET:** saturation region
- In these regions, transistors can provide **high voltage, current and power gains**



Transistor BJT Amplifier Concept

➤ The BJT is biased in **the active region** by dc voltage source V_{BE} .


➤ Total base-emitter voltage is:

$$V_{-BE} = V_{-BE} + v_{-be}$$

➤ Collector-emitter voltage is:


$$V_{CE} = V_{CC} - i_C R_C$$

$$I_C = \beta I_B$$

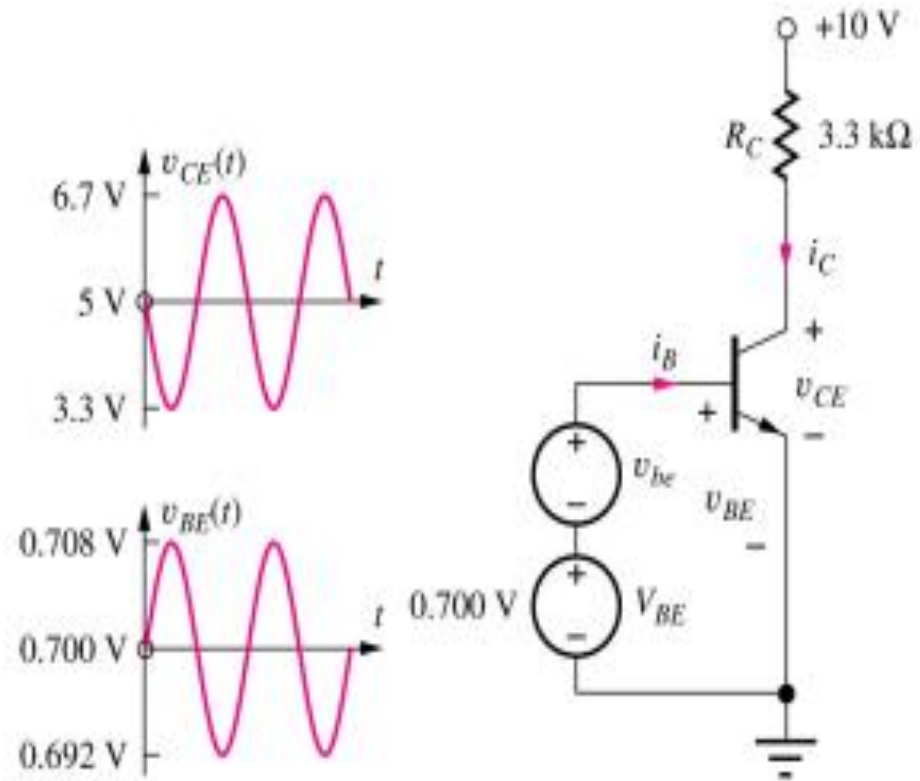

Transistor BJT Amplifier Concept

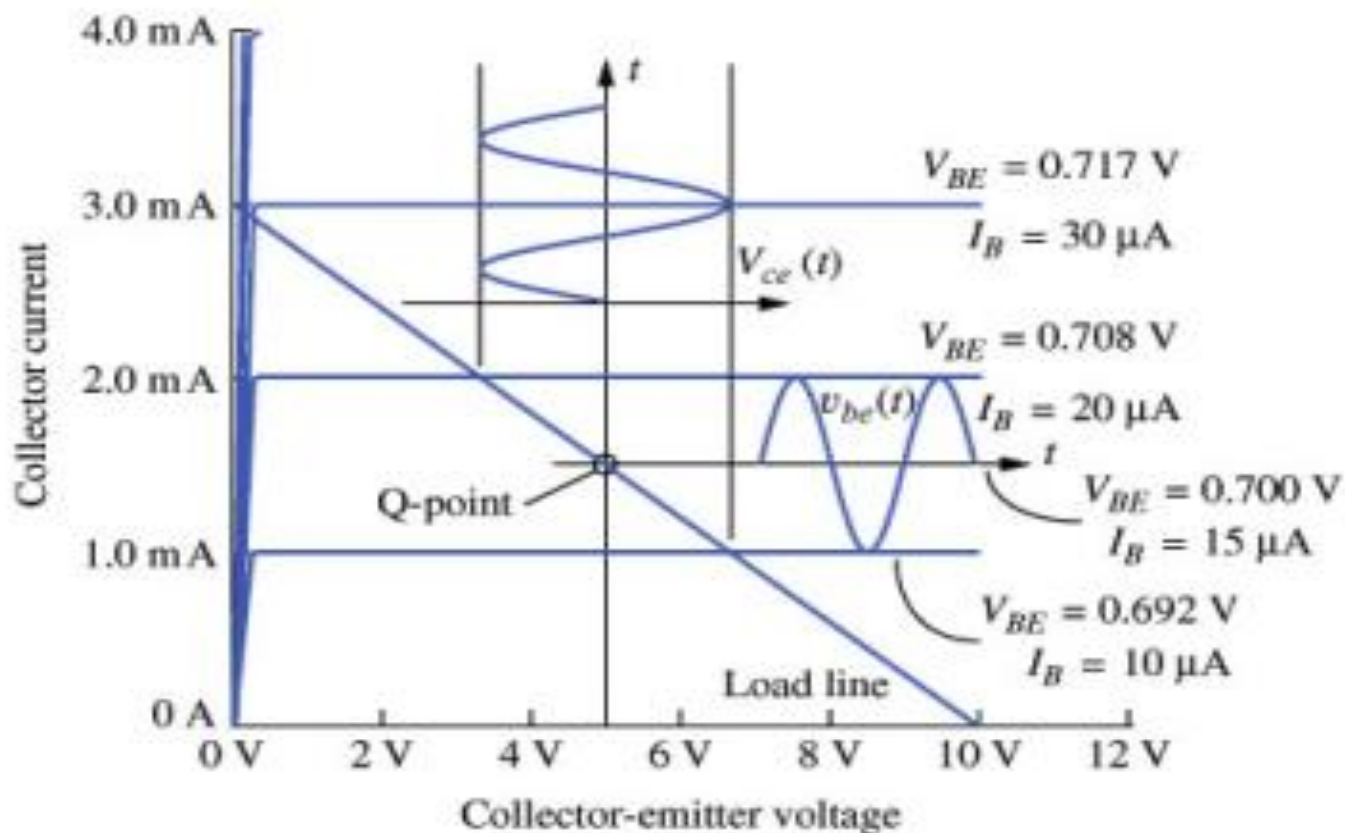- There are **180° phase shift** between the input and output signals.



Two Step Analysis:

➤ DC analysis:





- Find dc equivalent circuit by replacing **all capacitors by open circuits** and inductors by short circuits.
- Find Q-point from dc equivalent circuit by using appropriate large-signal transistor model.

➤ AC analysis:


- Find ac equivalent circuit by replacing **all capacitors by short circuits**, inductors by open circuits, dc voltage sources by ground connections and dc current sources by open circuits.
- Replace transistor by its small-signal model
- Use small-signal ac equivalent to analyze ac characteristics of amplifier.

Transistor dc Equivalent Circuit

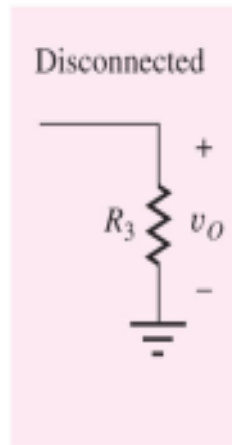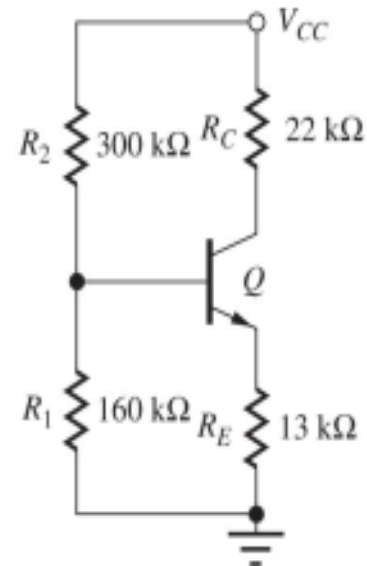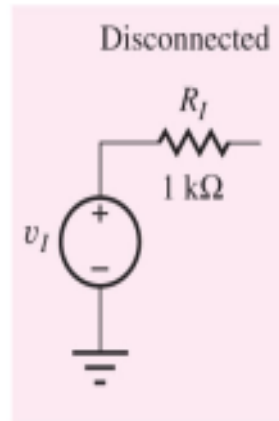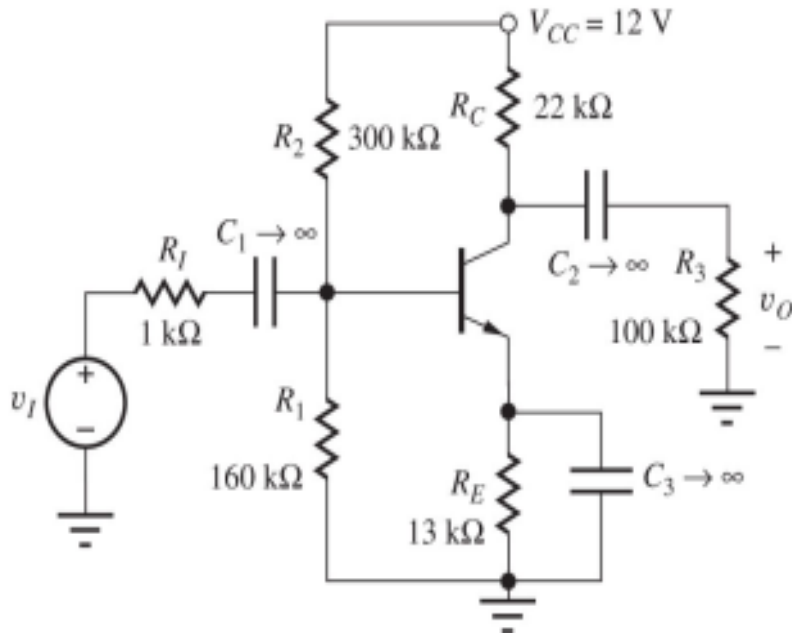All capacitors in the original amplifier circuit are replaced by open circuits, disconnecting v_i , R_i , and R_3 from circuit.



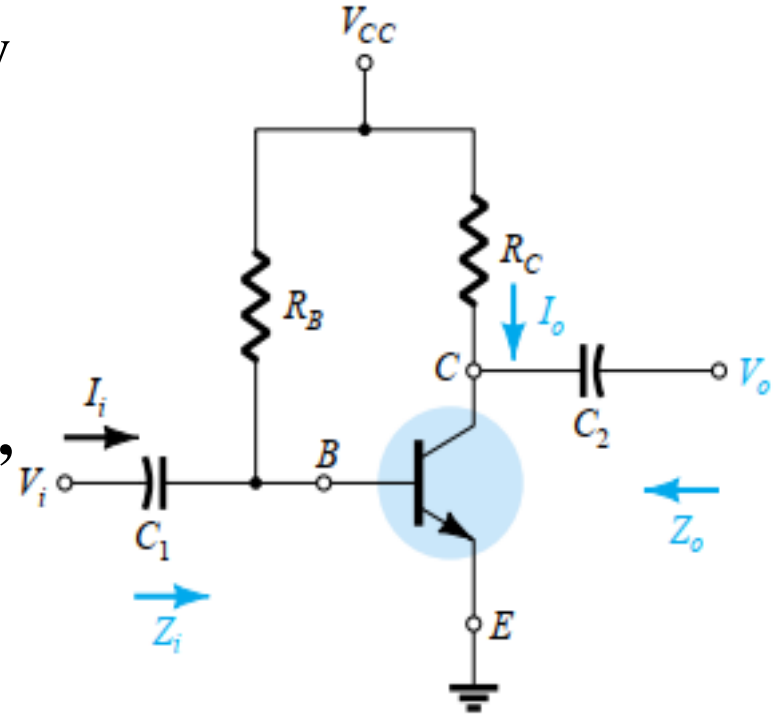- The small-signal ac analysis begins by removing the dc effects of V_{CC} .
- Blocking capacitors C_1 and C_2 by **short-circuit** equivalents, resulting in the network of Fig.
- Important network parameters Z_i , Z_o , I_i , and I_o .
- β , r_o : is typically obtained from a specification sheet.
- r_e : determined from a dc analysis of the system.




$$Z_i = R_B \parallel \beta r_e \quad \text{ohms}$$

R_B is greater than r_e by more than a factor of 10

$$Z_i \cong \beta r_e \quad \text{ohms}$$

$R_B \geq 10 \beta r_e$

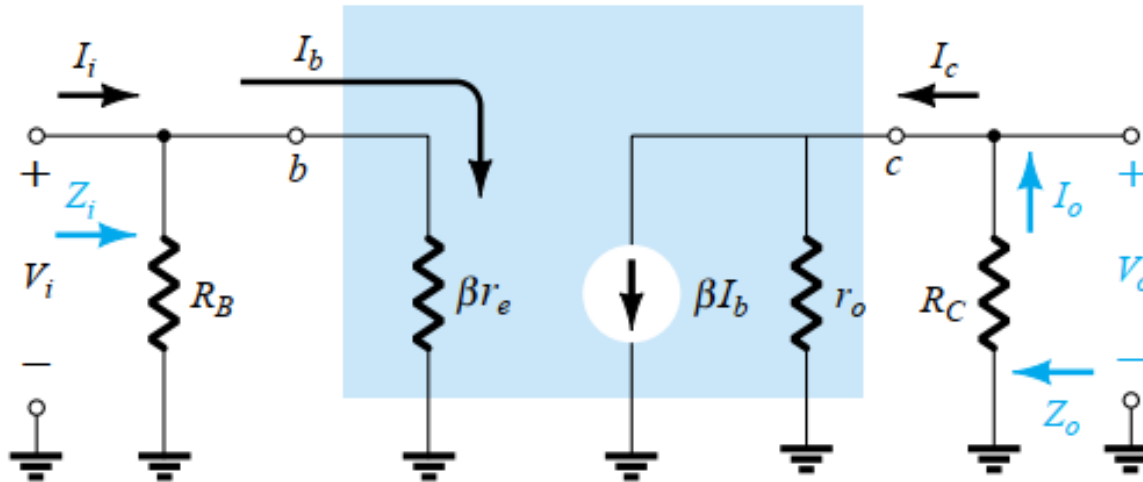

$$Z_o = R_C \parallel r_o \quad \text{ohms}$$

If $r_o \geq 10 R_C$, the approximation $R_C \parallel r_o \cong R_C$ is frequently applied.


$$Z_o \cong R_C \quad r_o \geq 10 R_C$$

$$V_o = -\beta I_b (R_C \parallel r_o) \quad I_b = \frac{V_i}{\beta r_c}$$

$$V_o = -\beta \left(\frac{V_i}{\beta r_e} \right) (R_C \parallel r_o)$$

$$A_v = \frac{V_o}{V_i} = -\frac{(R_C \parallel r_o)}{r_e}$$
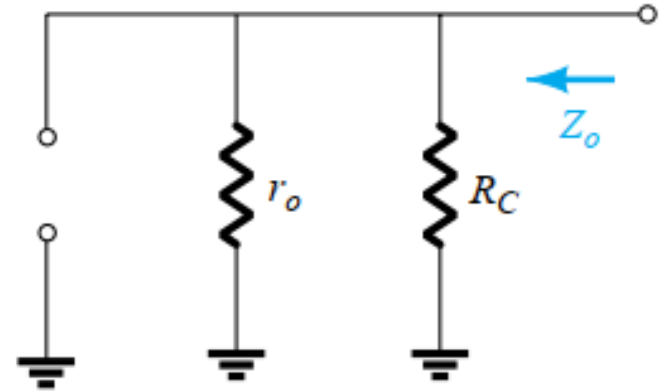
$$A_v = -\frac{R_C}{r_e} \quad r_o \geq 10 R_C$$



A_i : The current gain is determined in the following manner: Applying the current-divider rule to the input and output circuits,

$$I_o = \frac{(r_o)(\beta I_b)}{r_o + R_C} \quad \text{and} \quad \frac{I_o}{I_b} = \frac{r_o \beta}{r_o + R_C}$$

$$A_i = \frac{I_o}{I_i} = \left(\frac{I_o}{I_b} \right) \left(\frac{I_b}{I_i} \right) = \left(\frac{r_o \beta}{r_o + R_C} \right) \left(\frac{R_B}{R_B + \beta r_e} \right)$$

$$A_i = \frac{I_o}{I_i} = \frac{\beta R_B r_o}{(r_o + R_C)(R_B + \beta r_e)}$$

If $r_o \geq 10 R_C$ and $R_B \geq 10 \beta r_e$


$$A_i = \frac{I_o}{I_i} \cong \frac{\beta R_B r_o}{(r_o)(R_B)}$$

$$A_i \cong \beta$$




$$A_i = -A_v \frac{Z_i}{R_C}$$

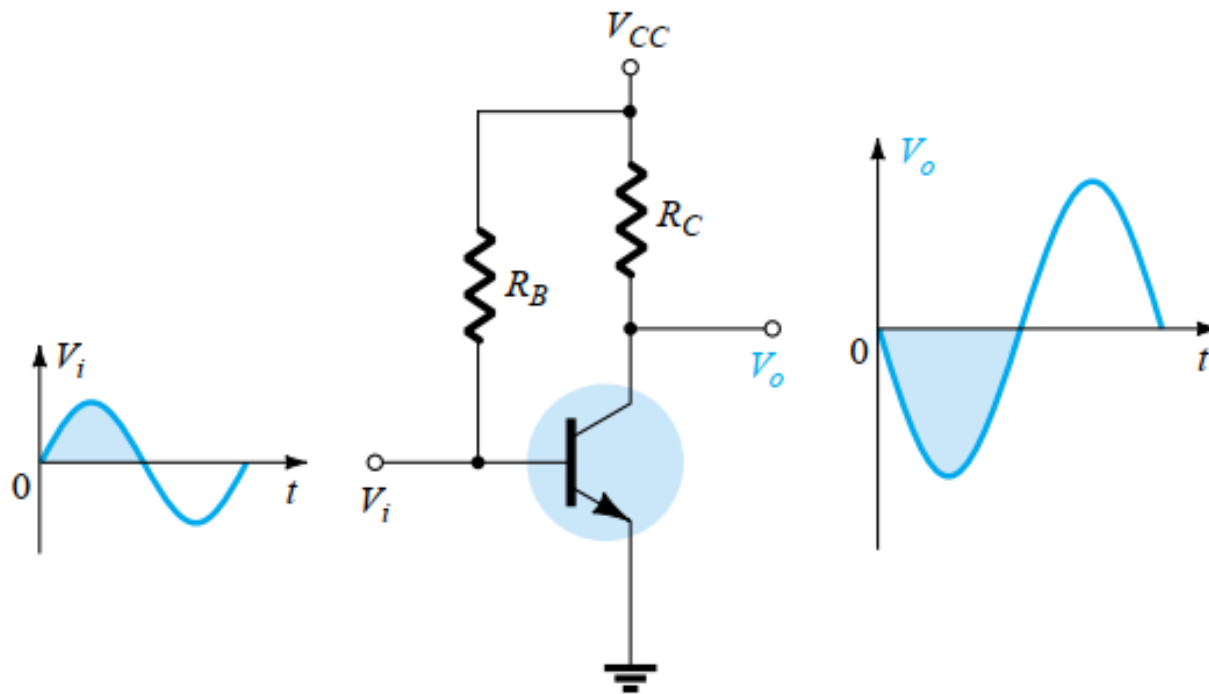Phase Relationship: The negative sign in the resulting equation for A_v reveals that a 180° phase shift occurs between the input and output signals, as shown in Fig



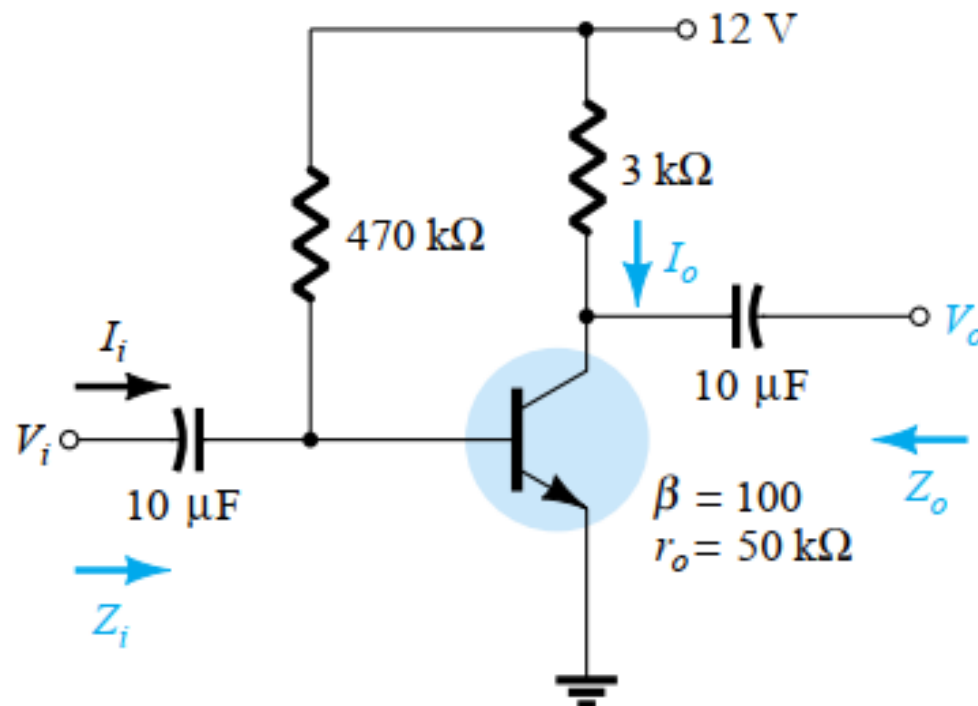Example

- Determine r_e .
- Find Z_i (with $r_o = \infty \Omega$).
- Calculate Z_o (with $r_o = \infty \Omega$).
- Determine A_v (with $r_o = \infty \Omega$).
- Find A_i (with $r_o = \infty \Omega$).
- Repeat parts (c) through (e) including $r_o = 50 \text{ k}\Omega$ in all calculations and compare results.



Example

(a) DC analysis:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{12 \text{ V} - 0.7 \text{ V}}{470 \text{ k}\Omega} = 24.04 \text{ }\mu\text{A}$$

$$I_E = (\beta + 1)I_B = (101)(24.04 \text{ }\mu\text{A}) = 2.428 \text{ mA}$$

$$r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{2.428 \text{ mA}} = \mathbf{10.71 \text{ }\Omega}$$

(b) $\beta r_e = (100)(10.71 \text{ }\Omega) = 1.071 \text{ k}\Omega$

$$Z_i = R_B \parallel \beta r_e = 470 \text{ k}\Omega \parallel 1.071 \text{ k}\Omega = \mathbf{1.069 \text{ k}\Omega}$$

(c) $Z_o = R_C = \mathbf{3 \text{ k}\Omega}$

(d) $A_v = -\frac{R_C}{r_e} = -\frac{3 \text{ k}\Omega}{10.71 \text{ }\Omega} = \mathbf{-280.11}$

(e) Since $R_B \geq 10\beta r_e (470 \text{ k}\Omega > 10.71 \text{ k}\Omega)$

$$A_i \cong \beta = \mathbf{100}$$

Example

$$(f) \quad Z_o = r_o \parallel R_C = 50 \text{ k}\Omega \parallel 3 \text{ k}\Omega = \mathbf{2.83 \text{ k}\Omega} \text{ vs. } 3 \text{ k}\Omega$$


$$A_v = -\frac{r_o \parallel R_C}{r_e} = \frac{2.83 \text{ k}\Omega}{10.71 \text{ }\Omega} = \mathbf{-264.24} \text{ vs. } -280.11$$

$$A_i = \frac{\beta R_B r_o}{(r_o + R_C)(R_B + \beta r_e)} = \frac{(100)(470 \text{ k}\Omega)(50 \text{ k}\Omega)}{(50 \text{ k}\Omega + 3 \text{ k}\Omega)(470 \text{ k}\Omega + 1.071 \text{ k}\Omega)} \\ = \mathbf{94.13} \text{ vs. } 100$$

As a check:

$$A_i = -A_v \frac{Z_i}{R_C} = \frac{-(-264.24)(1.069 \text{ k}\Omega)}{3 \text{ k}\Omega} = \mathbf{94.16}$$

Voltage-Divider Bias

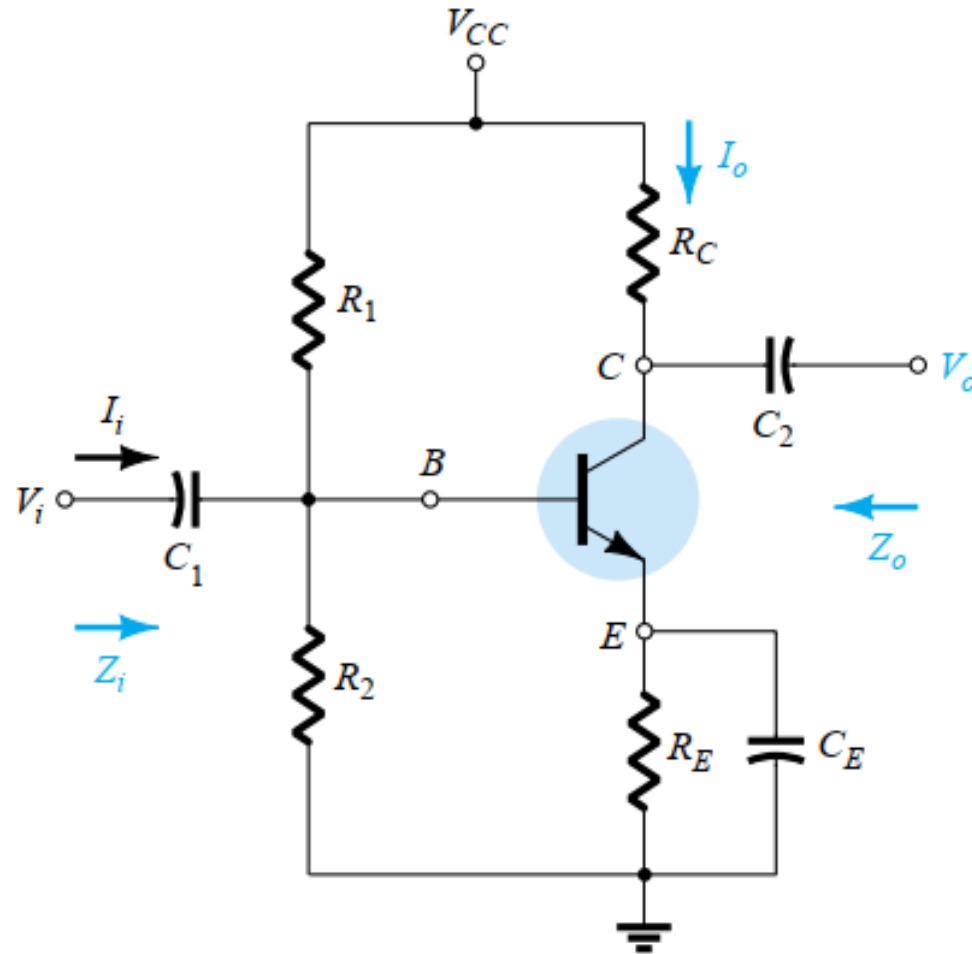


Voltage-Divider Bias

- The absence of R_E due to the low-impedance shorting effect of the bypass capacitor, C_E .

$$R' = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

$$Z_i = R' \parallel \beta r_e$$

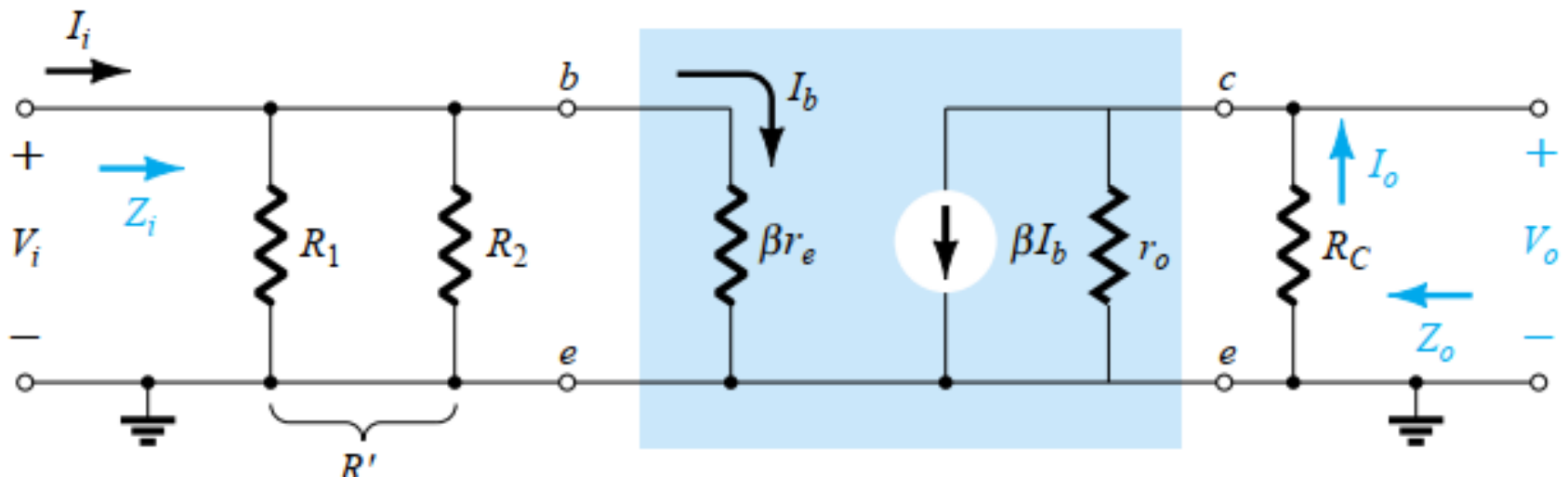

Voltage-Divider Bias

V_i set to 0 V resulting in $I_b = 0$ A and $\beta I_b = 0$ mA


$$Z_o = R_C \parallel r_o$$

If $r_o \geq 10 R_C$



$$Z_o \cong R_C$$

$r_o \geq 10 R_C$

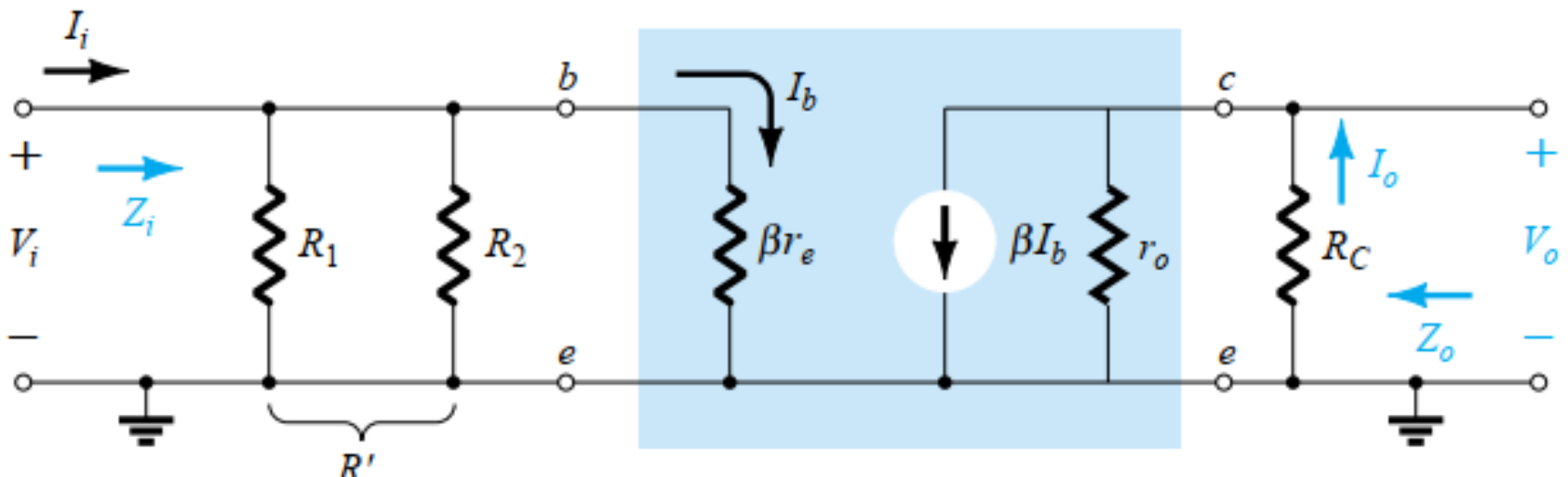

Voltage-Divider Bias


As: $R_C \parallel r_o$

$$V_o = -(\beta I_b)(R_C \parallel r_o)$$

$$I_b = \frac{V_i}{\beta r_e}$$

$$V_o = -\beta \left(\frac{V_i}{\beta r_e} \right) (R_C \parallel r_o)$$
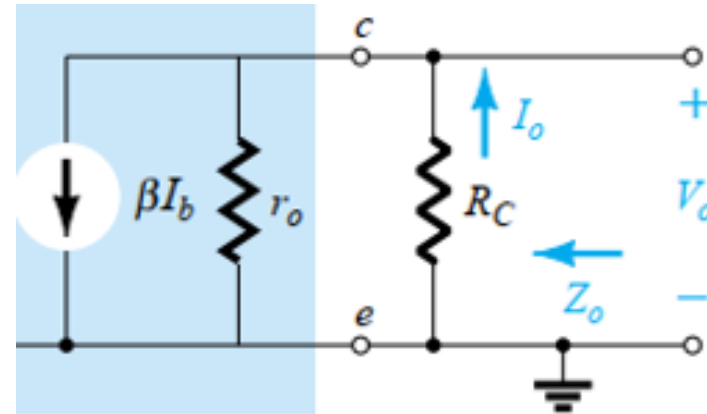
$$A_v = \frac{V_o}{V_i} = \frac{-R_C \parallel r_o}{r_e}$$



$$A_v = \frac{V_o}{V_i} \cong -\frac{R_C}{r_e}$$

$$r_o \geq 10R_C$$

Voltage-Divider Bias

$$A_i = \frac{I_o}{I_i} = \frac{\beta R' r_o}{(r_o + R_C)(R' + \beta r_e)}$$

If $r_o \geq 10 R_C \rightarrow A_i = \frac{I_o}{I_i} \cong \frac{\beta R' r_o}{r_o(R' + \beta r_e)}$

$$A_i = \frac{I_o}{I_i} \cong \frac{\beta R'}{R' + \beta r_e}$$

$r_o \geq 10 R_C$

If $R' \geq 10 \beta r_e \rightarrow A_i = \frac{I_o}{I_i} = \frac{\beta R'}{R'}$

$$A_i = \frac{I_o}{I_i} \cong \beta$$


$r_o \geq 10 R_C, R' \geq 10 \beta r_e$

$$A_i = -A_v \frac{Z_i}{R_C}$$

Example

For the network of Figure, determine:

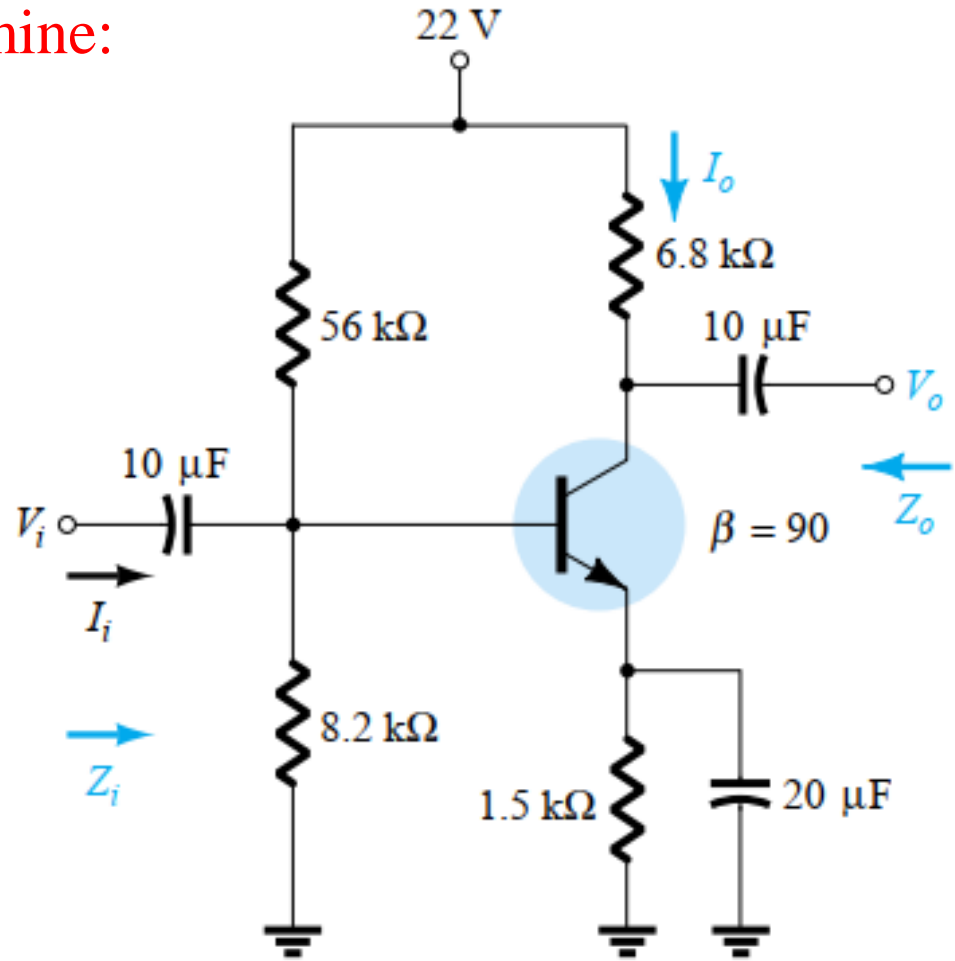- (a) r_e .
- (b) Z_i .
- (c) Z_o ($r_o = \infty \Omega$).
- (d) A_v ($r_o = \infty \Omega$).
- (e) A_i ($r_o = \infty \Omega$).



Example

(a) DC: Testing $\beta R_E > 10R_2$

$$(90)(1.5 \text{ k}\Omega) > 10(8.2 \text{ k}\Omega)$$

$$135 \text{ k}\Omega > 82 \text{ k}\Omega \text{ (satisfied)}$$

Using the approximate approach,

$$V_B = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{(8.2 \text{ k}\Omega)(22 \text{ V})}{56 \text{ k}\Omega + 8.2 \text{ k}\Omega} = 2.81 \text{ V}$$

$$V_E = V_B - V_{BE} = 2.81 \text{ V} - 0.7 \text{ V} = 2.11 \text{ V}$$

$$I_E = \frac{V_E}{R_E} = \frac{2.11 \text{ V}}{1.5 \text{ k}\Omega} = 1.41 \text{ mA}$$

$$r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{1.41 \text{ mA}} = \mathbf{18.44 \text{ }\Omega}$$

Example

$$(b) \ R' = R_1 \| R_2 = (56 \text{ k}\Omega) \| (8.2 \text{ k}\Omega) = 7.15 \text{ k}\Omega$$

$$\begin{aligned} Z_i &= R' \| \beta r_e = 7.15 \text{ k}\Omega \| (90)(18.44 \text{ }\Omega) = 7.15 \text{ k}\Omega \| 1.66 \text{ k}\Omega \\ &= \mathbf{1.35 \text{ k}\Omega} \end{aligned}$$

$$(c) \ Z_o = R_C = \mathbf{6.8 \text{ k}\Omega}$$

$$(d) \ A_v = -\frac{R_C}{r_e} = -\frac{6.8 \text{ k}\Omega}{18.44 \text{ }\Omega} = \mathbf{-368.76}$$

(e) The condition $R' \geq 10\beta r_e$ ($7.15 \text{ k}\Omega \geq 10(1.66 \text{ k}\Omega) = 16.6 \text{ k}\Omega$) is *not* satisfied. Therefore,

$$A_i \cong \frac{\beta R'}{R' + \beta r_e} = \frac{(90)(7.15 \text{ k}\Omega)}{7.15 \text{ k}\Omega + 1.66 \text{ k}\Omega} = \mathbf{73.04}$$

CE Emitter-Bias Configuration

$$V_i = I_b \beta r_e + I_e R_E$$

$$V_i = I_b \beta r_e + (\beta + 1) I_b R_E$$

$$Z_b = \frac{V_i}{I_b} = \beta r_e + (\beta + 1) R_E$$

$$Z_b = \beta r_e + (\beta + 1) R_E$$


$$Z_b \cong \beta r_e + \beta R_E$$

$$Z_b \cong \beta (r_e + R_E)$$

$$R_E \gg r_e$$



$$Z_b \cong \beta R_E$$

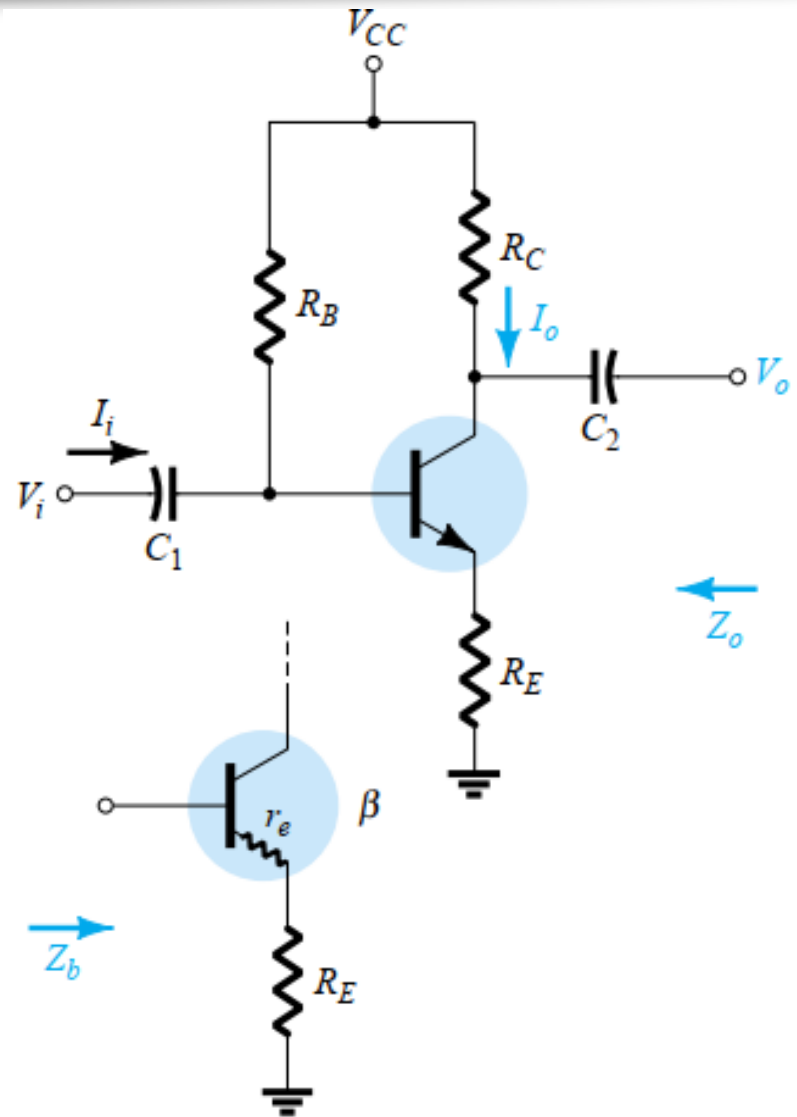

CE Emitter-Bias Configuration

$$Z_i = R_B \parallel Z_b$$

$$Z_o = R_C$$

$$I_b = \frac{V_i}{Z_b}$$

$$V_o = -I_o R_C = -\beta I_b R_C$$


$$= -\beta \left(\frac{V_i}{Z_b} \right) R_C$$

$$A_v = \frac{V_o}{V_i} = -\frac{\beta R_C}{Z_b}$$

$$A_v = \frac{V_o}{V_i} = -\frac{R_C}{r_e + R_E}$$

$$A_v = \frac{V_o}{V_i} \cong -\frac{R_C}{R_E}$$

$$Z_b \cong \beta R_E,$$

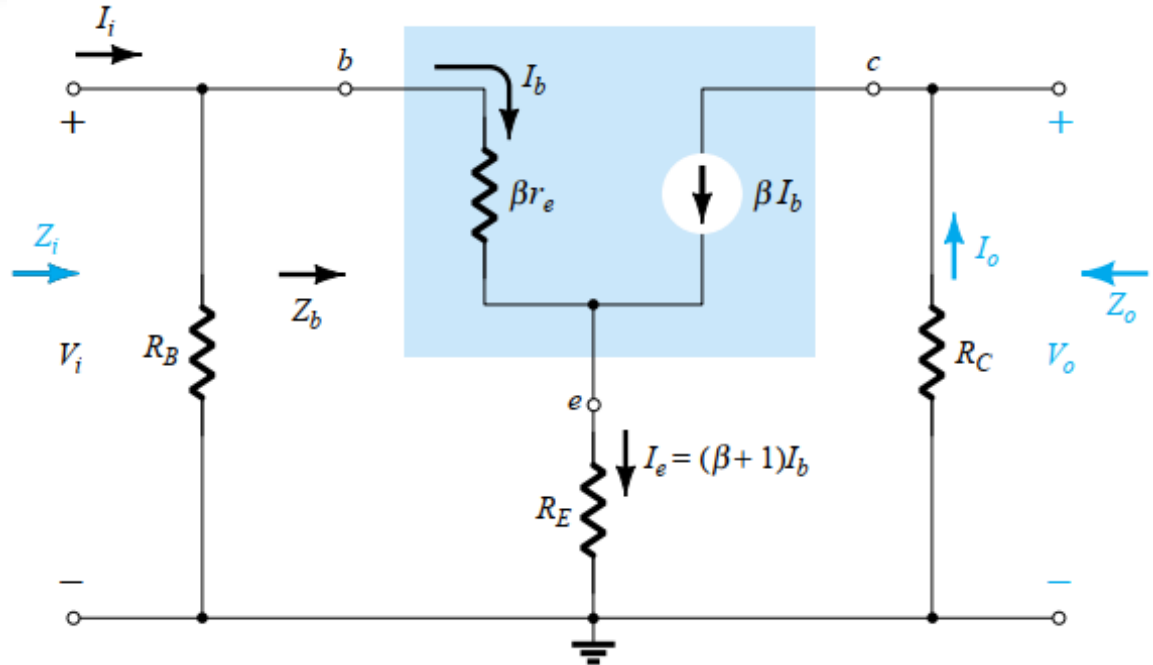

CE Emitter-Bias Configuration

To obtain A_i

➤ Applying the current-divider rule to the input circuit will result in:

$$I_b = \frac{R_B I_i}{R_B + Z_b}$$

$$\frac{I_b}{I_i} = \frac{R_B}{R_B + Z_b}$$

$$I_o = \beta I_b$$

$$\frac{I_o}{I_b} = \beta$$

$$A_i = \frac{I_o}{I_i} = \frac{I_o}{I_b} \frac{I_b}{I_i}$$

$$= \beta \frac{R_B}{R_B + Z_b}$$

$$A_i = \frac{I_o}{I_i} = \frac{\beta R_B}{R_B + Z_b}$$

$$A_i = -A_v \frac{Z_i}{R_C}$$

Phase relationship: The negative sign in reveals a 180° phase shift between V_o and V_i .

CE Emitter-Bias Configuration

Z_i :

$$Z_b = \beta r_e + \left[\frac{(\beta + 1) + R_C/r_o}{1 + (R_C + R_E)/r_o} \right] R_E$$

Since the ratio R_C/r_o is always much less than $(\beta + 1)$,

$$Z_b \cong \beta r_e + \frac{(\beta + 1)R_E}{1 + (R_C + R_E)/r_o}$$

For $r_o \geq 10(R_C + R_E)$,

$$Z_b \cong \beta r_e + (\beta + 1)R_E$$

For $r_o \geq 10(R_C + R_E)$,

$$Z_b \cong \beta r_e + (\beta + 1)R_E$$

$$Z_b \cong \beta(r_e + R_E)$$

$r_o \geq 10(R_C + R_E)$

CE Emitter-Bias Configuration

Z_o :

$$Z_o = R_C \parallel \left[r_o + \frac{\beta(r_o + r_e)}{1 + \frac{\beta r_e}{R_E}} \right]$$

$$Z_o \cong R_C \parallel r_o \left[1 + \frac{\beta}{1 + \frac{\beta r_e}{R_E}} \right]$$

$$Z_o \cong R_C \parallel r_o \left[1 + \frac{1}{\frac{1}{\beta} + \frac{r_e}{R_E}} \right]$$

$R_E \gg \beta$ and r_o :

$$Z_o = R_C$$

CE Emitter-Bias Configuration

A_v :

$$A_v = \frac{V_o}{V_i} = \frac{-\frac{\beta R_C}{Z_b} \left[1 + \frac{r_e}{r_o} \right] + \frac{R_C}{r_o}}{1 + \frac{R_C}{r_o}}$$

The ratio $\frac{r_e}{r_o} \ll 1$

and

$$A_v = \frac{V_o}{V_i} \cong \frac{-\frac{\beta R_C}{Z_b} + \frac{R_C}{r_o}}{1 + \frac{R_C}{r_o}}$$

For $r_o \geq 10R_C$,

$$A_v = \frac{V_o}{V_i} \cong -\frac{\beta R_C}{Z_b}$$


$r_o \geq 10R_C$

$$A_i = -A_v \frac{Z_i}{R_C}$$

Example

For the network of shown figure, without C_E (un bypassed), determine:

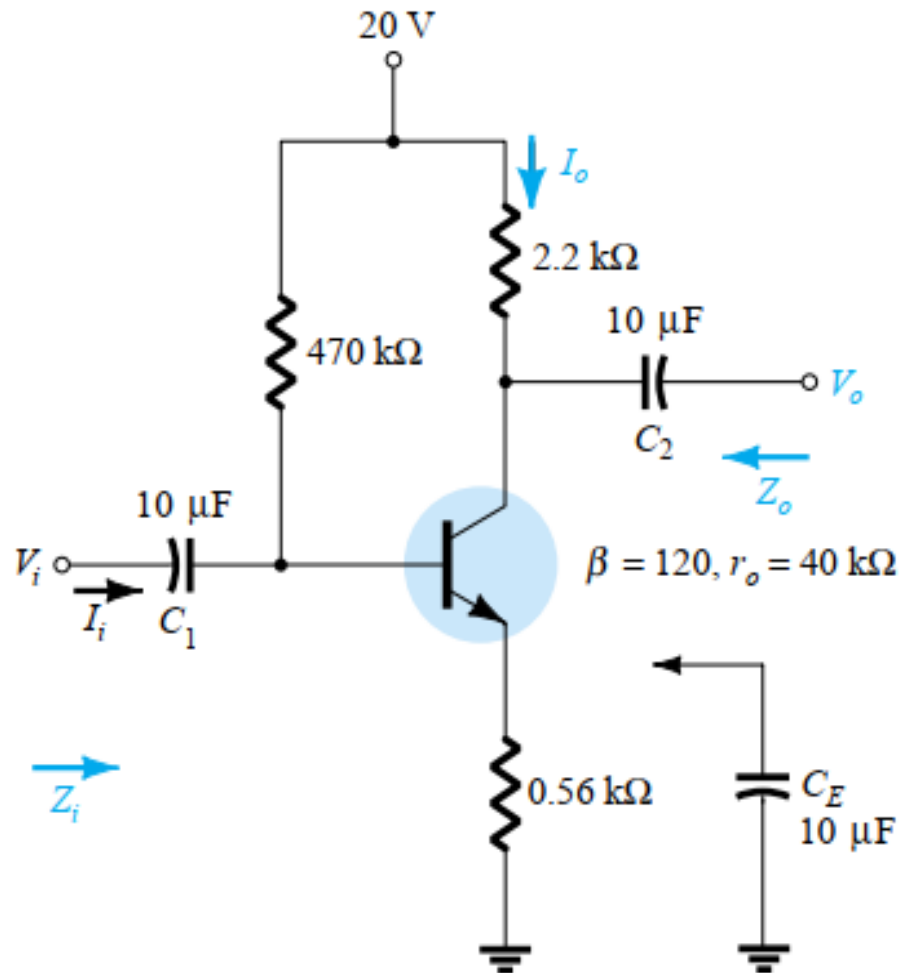- (a) r_e .
- (b) Z_i .
- (c) Z_o .
- (d) A_v .
- (e) A_i .



Example

$$(a) \text{ DC: } I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E} = \frac{20 \text{ V} - 0.7 \text{ V}}{470 \text{ k}\Omega + (121)0.56 \text{ k}\Omega} = 35.89 \mu\text{A}$$

$$I_E = (\beta + 1)I_B = (121)(46.5 \mu\text{A}) = 4.34 \text{ mA}$$

$$\text{and } r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{4.34 \text{ mA}} = \mathbf{5.99 \Omega}$$

(b) Testing the condition $r_o \geq 10(R_C + R_E)$,

$$40 \text{ k}\Omega \geq 10(2.2 \text{ k}\Omega + 0.56 \text{ k}\Omega)$$

$$40 \text{ k}\Omega \geq 10(2.76 \text{ k}\Omega) = 27.6 \text{ k}\Omega \text{ (satisfied)}$$

Therefore,

$$\begin{aligned} Z_b &\cong \beta(r_e + R_E) = 120(5.99 \Omega + 560 \Omega) \\ &= 67.92 \text{ k}\Omega \end{aligned}$$

and

$$\begin{aligned} Z_i &= R_B \parallel Z_b = 470 \text{ k}\Omega \parallel 67.92 \text{ k}\Omega \\ &= \mathbf{59.34 \text{ k}\Omega} \end{aligned}$$

Example

(c) $Z_o = R_C = \mathbf{2.2\text{ k}\Omega}$



(d) $r_o \geq 10R_C$ is satisfied. Therefore,

$$A_v = \frac{V_o}{V_i} \cong -\frac{\beta R_C}{Z_b} = -\frac{(120)(2.2\text{ k}\Omega)}{67.92\text{ k}\Omega}$$
$$= \mathbf{-3.89}$$

(e) $A_i = -A_v \frac{Z_i}{R_C} = -(-3.89) \left(\frac{59.34\text{ k}\Omega}{2.2\text{ k}\Omega} \right)$

$$= \mathbf{104.92}$$

Emitter-follower Configuration

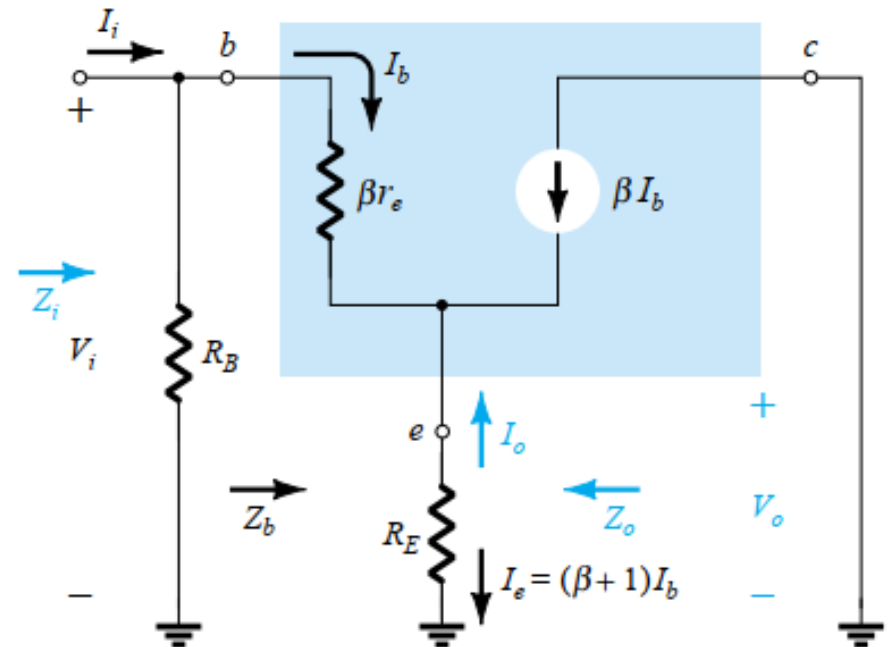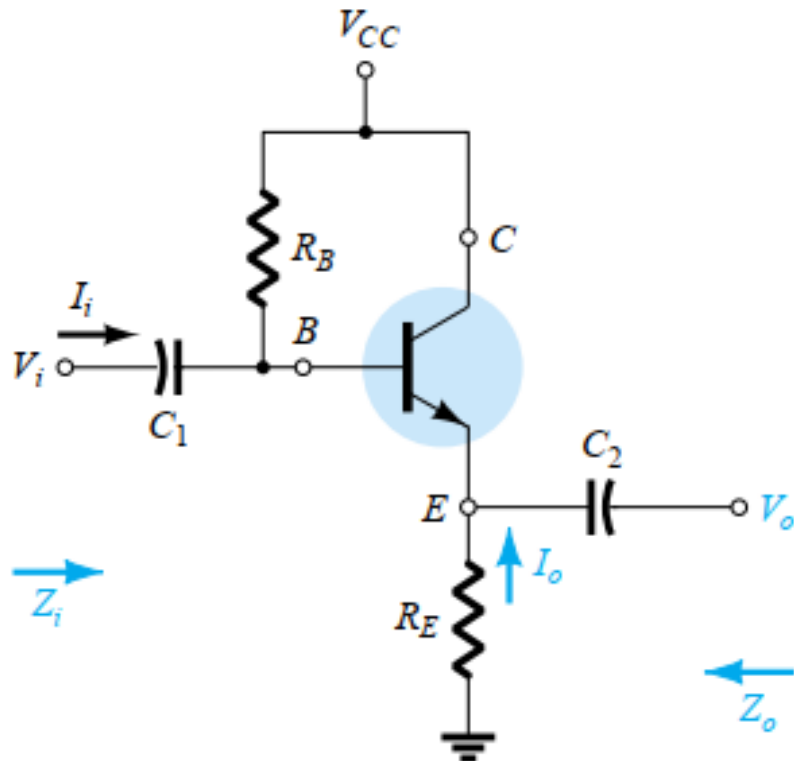

Emitter-follower Configuration

Z_i :

$$Z_i = R_B \parallel Z_b$$

$$Z_b \cong \beta(r_e + R_E)$$

$$Z_b = \beta r_e + (\beta + 1)R_E$$

$$Z_b \cong \beta R_E$$

Z_o :


$$I_b = \frac{V_i}{Z_b}$$

$$I_e = (\beta + 1)I_b = (\beta + 1) \frac{V_i}{Z_b}$$

$$I_e = \frac{(\beta + 1)V_i}{\beta r_e + (\beta + 1)R_E}$$

$$I_e = \frac{V_i}{\left[\frac{\beta r_e}{(\beta + 1)} \right] + R_E}$$

$$(\beta + 1) \cong \beta$$

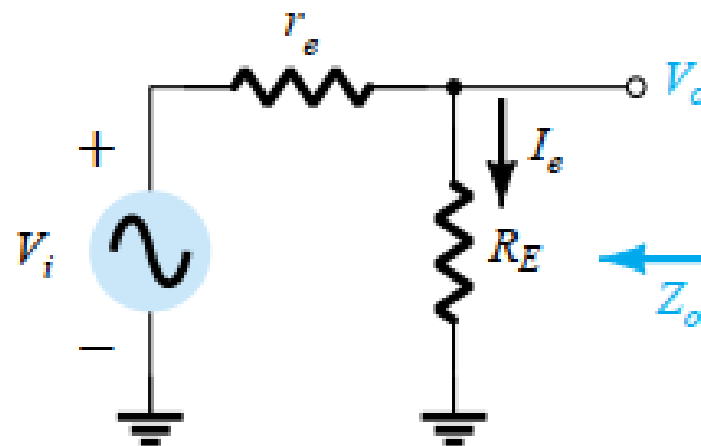

Emitter-follower Configuration

$$\frac{\beta r_e}{\beta + 1} \cong \frac{\beta r_e}{\beta} = r_e$$

$$I_e \cong \frac{V_i}{r_e + R_E}$$

$$Z_o = R_E \parallel r_e$$


$$Z_o \cong r_e$$

$$A_v: V_o = \frac{R_E V_i}{R_E + r_e}$$

$$A_v = \frac{V_o}{V_i} = \frac{R_E}{R_E + r_e}$$

R_E is usually much greater than r_e , $R_E + r_e \cong R_E$

$$A_v = \frac{V_o}{V_i} \cong 1$$

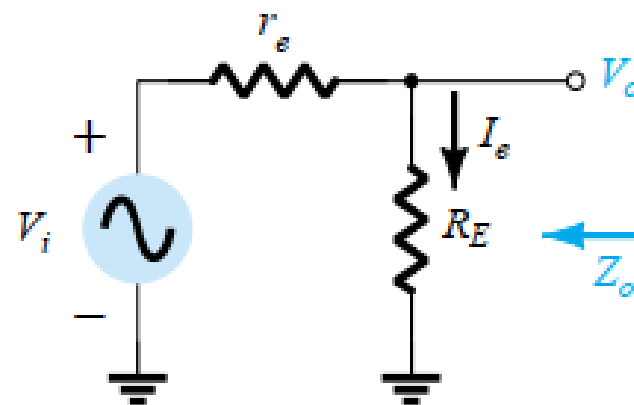

Emitter-follower Configuration

A_i :

$$I_b = \frac{R_B I_i}{R_B + Z_b}$$

$$\frac{I_b}{I_i} = \frac{R_B}{R_B + Z_b}$$

$$A_i = \frac{I_o}{I_i} = \frac{I_o}{I_b} \frac{I_b}{I_i}$$

$$= -(\beta + 1) \frac{R_B}{R_B + Z_b}$$

$$A_i \cong -\frac{\beta R_B}{R_B + Z_b}$$

$$I_o = -I_e = -(\beta + 1)I_b$$

$$\frac{I_o}{I_b} = -(\beta + 1)$$

$$A_i = -A_v \frac{Z_i}{R_E}$$

Emitter-follower Configuration

Z_o :

$$Z_o = r_o \parallel R_E \parallel \frac{\beta r_e}{(\beta + 1)}$$

Using $\beta + 1 \cong \beta$, $\rightarrow Z_o = r_o \parallel R_E \parallel r_e$

$$Z_o \cong R_E \parallel r_e$$

Any r_o

A_v :

$$A_v = \frac{(\beta + 1)R_E / Z_b}{1 + \frac{R_E}{r_o}}$$

If the condition $r_o \geq 10R_E$ is satisfied and we use the approximation $\beta + 1 \cong \beta$,

$$A_v \cong \frac{\beta R_E}{Z_b} \quad Z_b \cong \beta(r_e + R_E) \quad A_v \cong \frac{\beta R_E}{\beta(r_e + R_E)}$$


$$A_v \cong \frac{R_E}{r_e + R_E}$$

$r_o \geq 10R_E$

Example

For the emitter-follower network of Figure, determine:

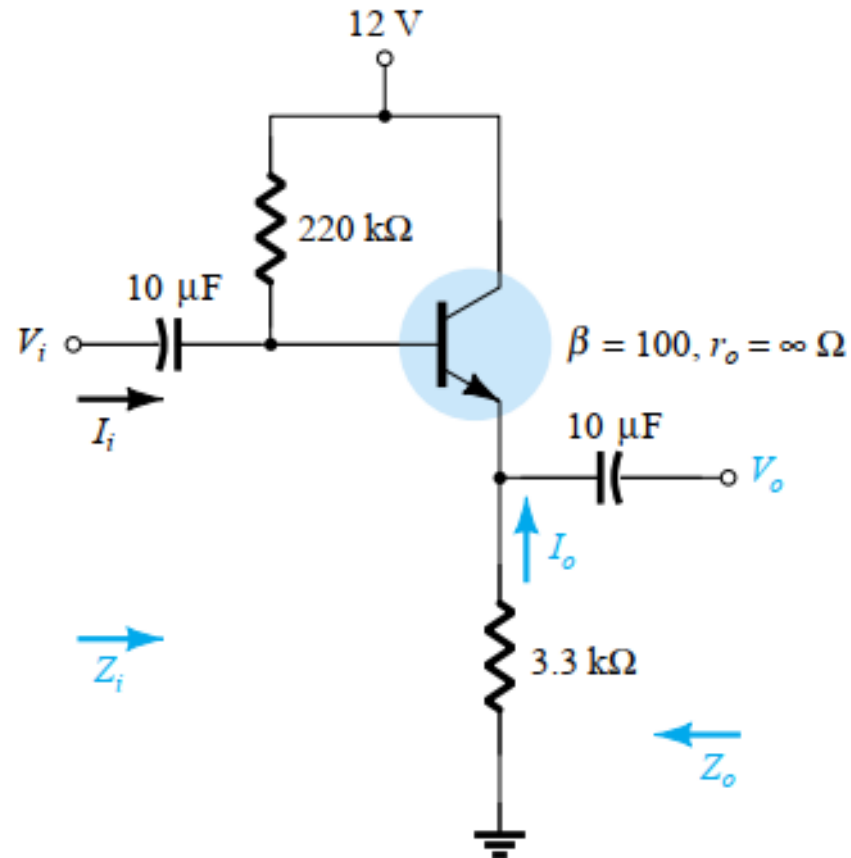- (a) r_e .
- (b) Z_i .
- (c) Z_o .
- (d) A_v .
- (e) A_i .



Example

$$\begin{aligned} \text{(a)} \quad I_B &= \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E} \\ &= \frac{12 \text{ V} - 0.7 \text{ V}}{220 \text{ k}\Omega + (101)3.3 \text{ k}\Omega} = 20.42 \text{ }\mu\text{A} \end{aligned}$$

$$\begin{aligned} I_E &= (\beta + 1)I_B \\ &= (101)(20.42 \text{ }\mu\text{A}) = 2.062 \text{ mA} \end{aligned}$$

$$r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{2.062 \text{ mA}} = \mathbf{12.61 \text{ }\Omega}$$

$$\begin{aligned} \text{(b)} \quad Z_b &= \beta r_e + (\beta + 1)R_E \\ &= (100)(12.61 \text{ }\Omega) + (101)(3.3 \text{ k}\Omega) \\ &= 1.261 \text{ k}\Omega + 333.3 \text{ k}\Omega \\ &= 334.56 \text{ k}\Omega \cong \beta R_E \end{aligned}$$

$$\begin{aligned} Z_i &= R_B \parallel Z_b = 220 \text{ k}\Omega \parallel 334.56 \text{ k}\Omega \\ &= \mathbf{132.72 \text{ k}\Omega} \end{aligned}$$

Example

$$(c) \quad Z_o = R_E \parallel r_e = 3.3 \text{ k}\Omega \parallel 12.61 \text{ }\Omega$$

$$= \mathbf{12.56 \text{ }\Omega} \cong r_e$$

$$(d) \quad A_v = \frac{V_o}{V_i} = \frac{R_E}{R_E + r_e} = \frac{3.3 \text{ k}\Omega}{3.3 \text{ k}\Omega + 12.61 \text{ }\Omega}$$


$$= \mathbf{0.996} \cong 1$$

$$(e) \quad A_i \cong -\frac{\beta R_B}{R_B + Z_b} = -\frac{(100)(220 \text{ k}\Omega)}{220 \text{ k}\Omega + 334.56 \text{ k}\Omega} = \mathbf{-39.67}$$

$$A_i = -A_v \frac{Z_i}{R_E} = -(0.996) \left(\frac{132.72 \text{ k}\Omega}{3.3 \text{ k}\Omega} \right) = \mathbf{-40.06}$$

Common-base Configuration

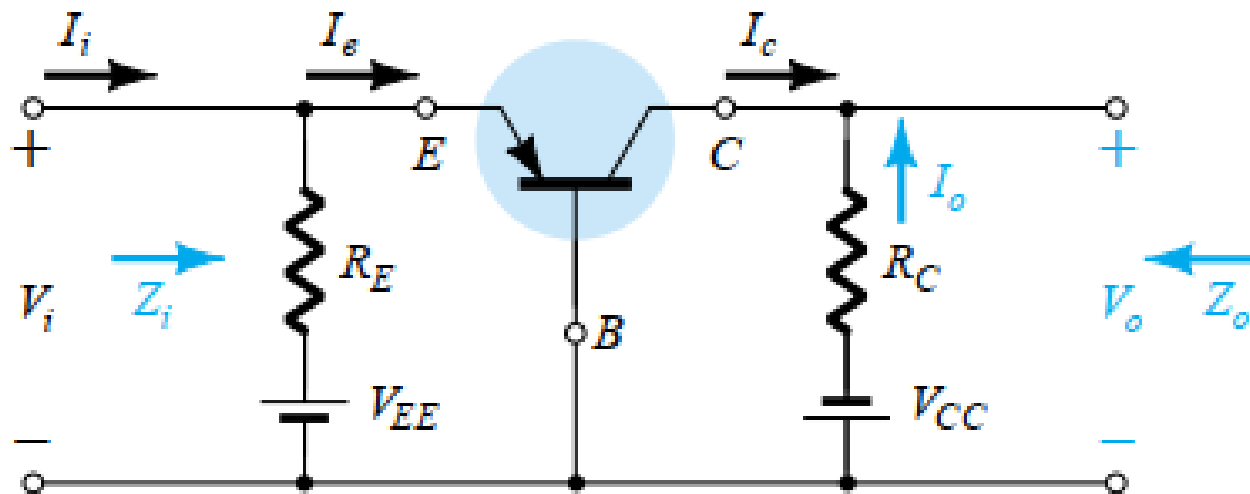- Low input impedance.
- High output impedance.
- Current gain less than 1.
- Voltage gain quite large.



Common-base Configuration


$$Z_i = R_E \parallel r_e$$

$$Z_o = R_C$$

$$V_o = -I_o R_C = -(-I_e) R_C = \alpha I_e R_C \qquad I_e = \frac{V_i}{r_e}$$


$$V_o = \alpha \left(\frac{V_i}{r_e} \right) R_C$$
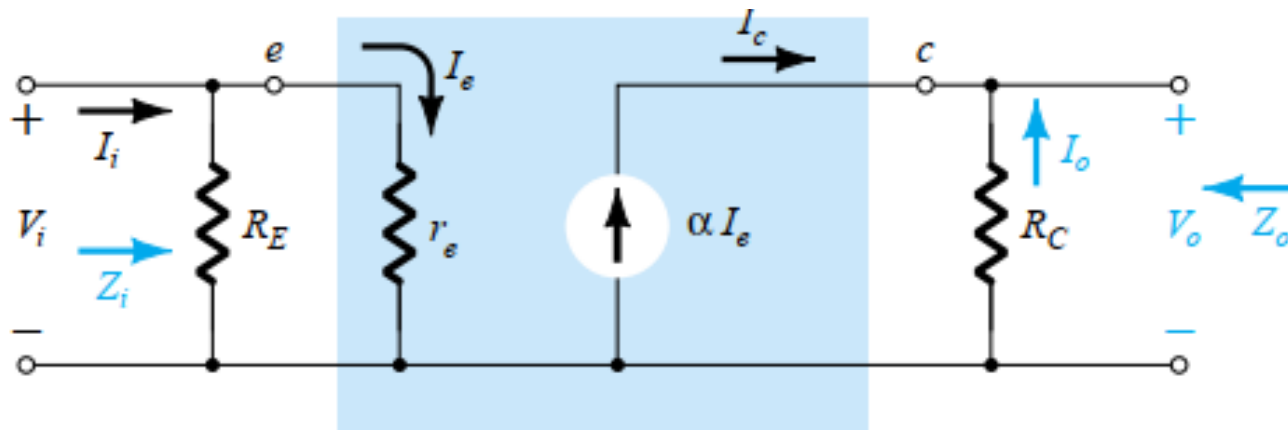
$$A_v = \frac{V_o}{V_i} = \frac{\alpha R_C}{r_e} \cong \frac{R_C}{r_e}$$



Common-base Configuration


$$R_E \gg r_e$$

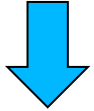

$$I_e = I_i$$

$$I_o = -\alpha I_e = -\alpha I_i$$

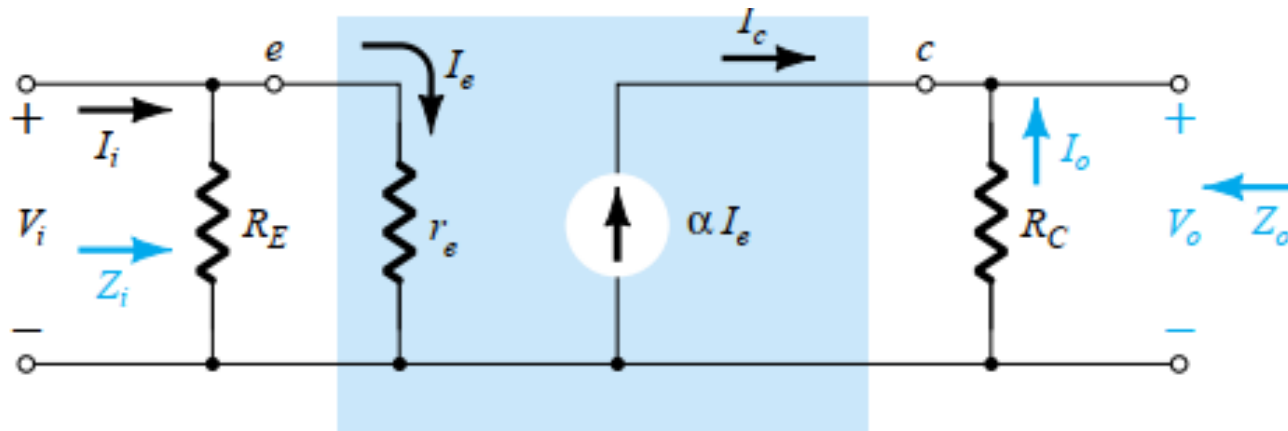
$$A_i = \frac{I_o}{I_i} = -\alpha \cong -1$$



Example

For the network of Figure, determine:

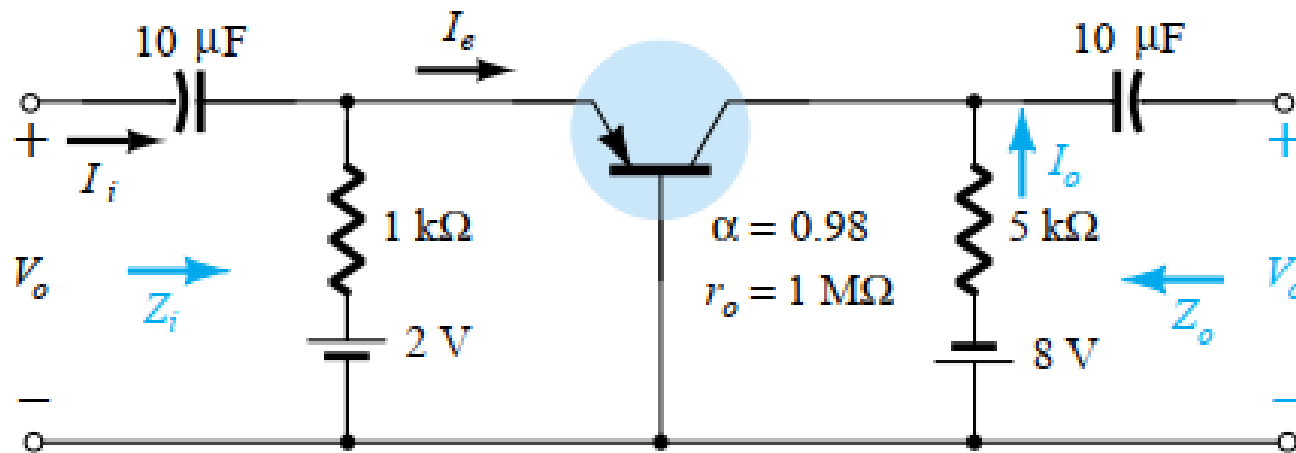- (a) r_e .
- (b) Z_i .
- (c) Z_o .
- (d) A_v .
- (e) A_i .



Example

$$(a) \quad I_E = \frac{V_{EE} - V_{BE}}{R_E} = \frac{2 \text{ V} - 0.7 \text{ V}}{1 \text{ k}\Omega} = \frac{1.3 \text{ V}}{1 \text{ k}\Omega} = 1.3 \text{ mA}$$

$$r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{1.3 \text{ mA}} = \mathbf{20 \text{ }\Omega}$$

$$(b) \quad Z_i = R_E \parallel r_e = 1 \text{ k}\Omega \parallel 20 \text{ }\Omega \\ = \mathbf{19.61 \text{ }\Omega} \cong r_e$$

$$(c) \quad Z_o = R_C = \mathbf{5 \text{ k}\Omega}$$

$$(d) \quad A_v \cong \frac{R_C}{r_e} = \frac{5 \text{ k}\Omega}{20 \text{ }\Omega} = \mathbf{250}$$

$$(e) \quad A_i = \mathbf{-0.98} \cong -1$$

THANK
YOU

